

# Voltage Regulators

## Analog Electronics Lab Experiment - 10

**Submitted by :** Jash Shah

**BITS Id :** 2018A8PS0507P

**Lab Section:** P5

**Submitted to :** Sambhavi Shukla, Teena Gakhar

**Date :** 15/4/21

---

### **1. Objective**


To study the operation of fixed and adjustable voltage regulators using LM723, in LTSpice.

Upload a single PDF file on Nalanda which includes


- 1) Circuit diagrams for both low and high voltage regulators.
- 2) Show  $I(\text{out})$  and  $V(\text{out})$  in tabular form for both circuits.

## 2. High Voltage Regulators


### 1. Circuit Diagram:

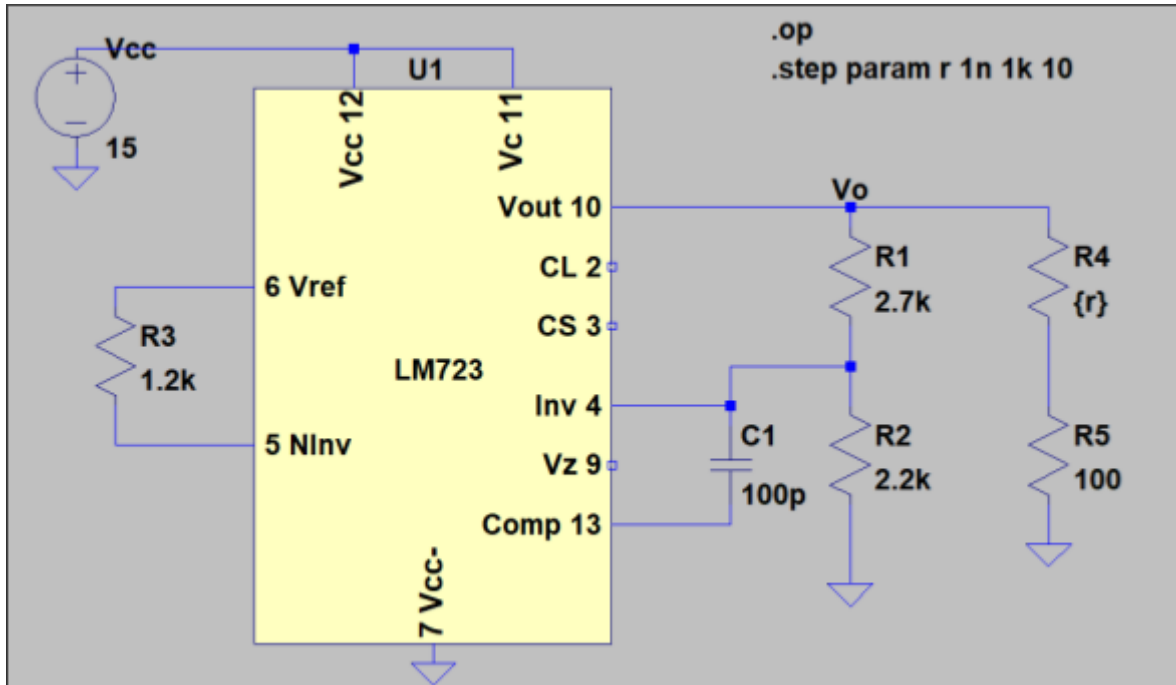

## 2. Resultant Curve for current

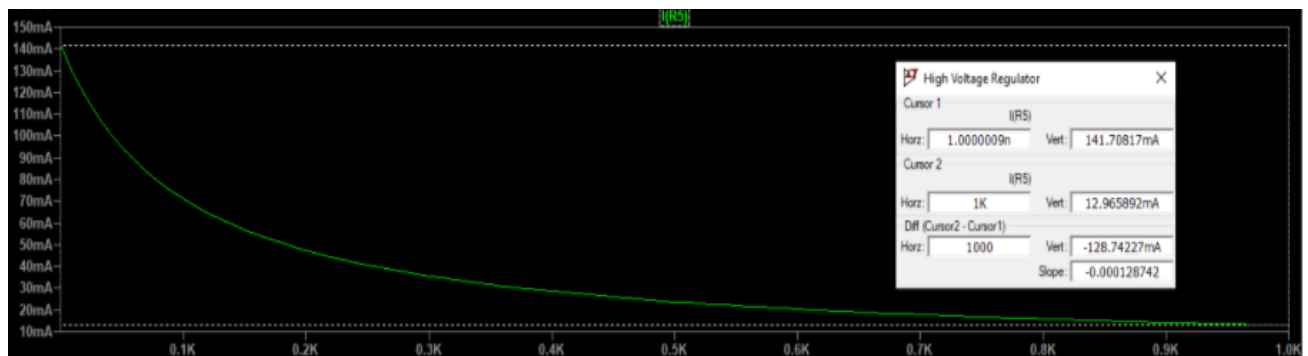


### 3. Resultant Curve for Voltage

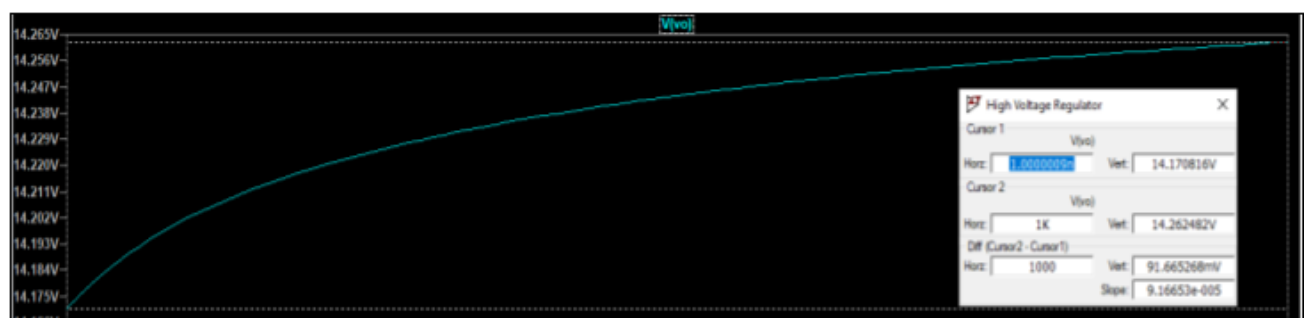


### 3. Low Voltage Regulators


### 1. Circuit Diagram:

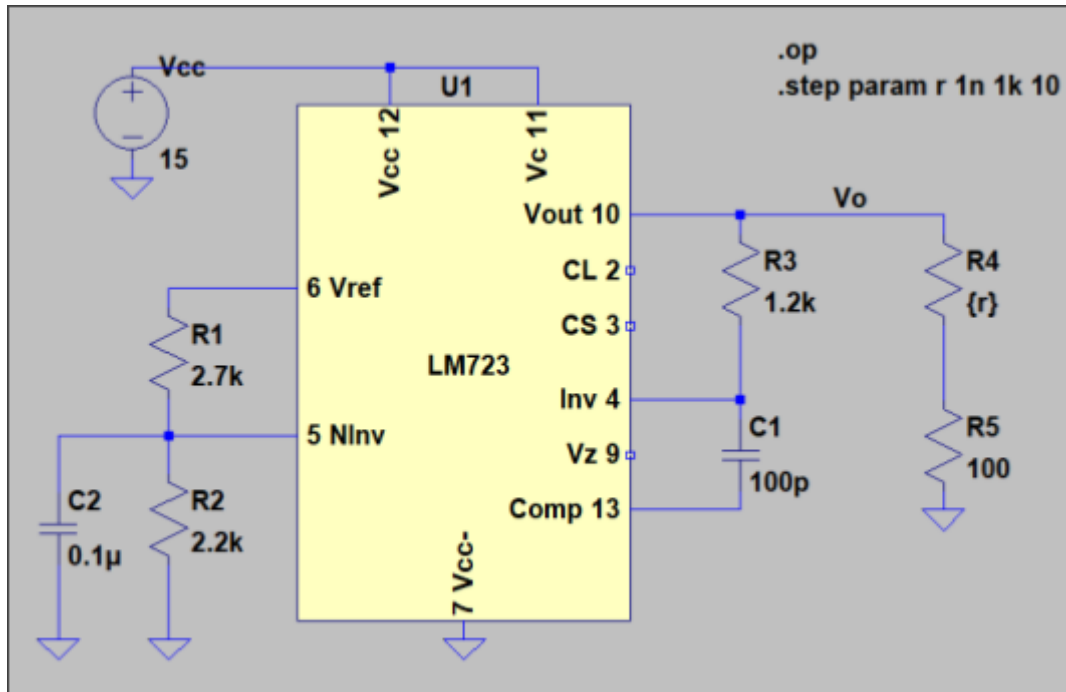

## 2. Resultant Curve for current

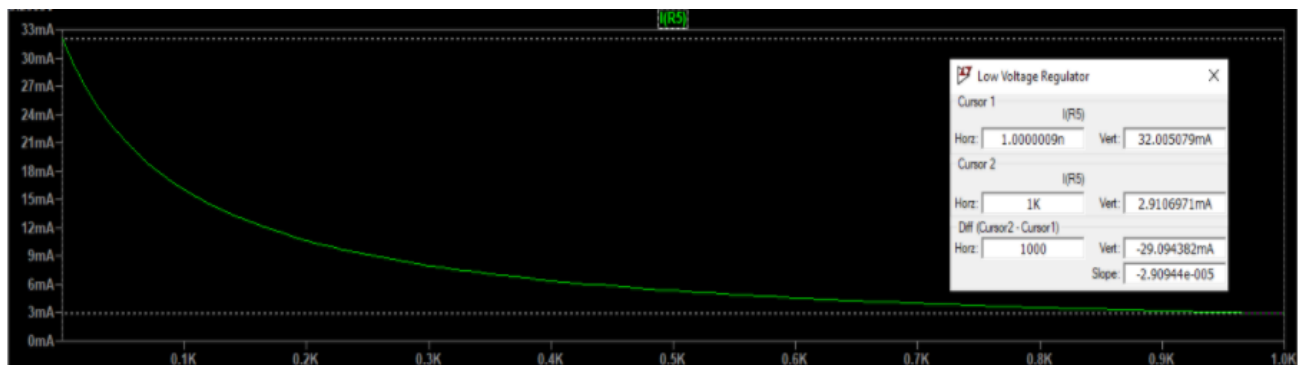

### 3. Resultant Curve for Voltage

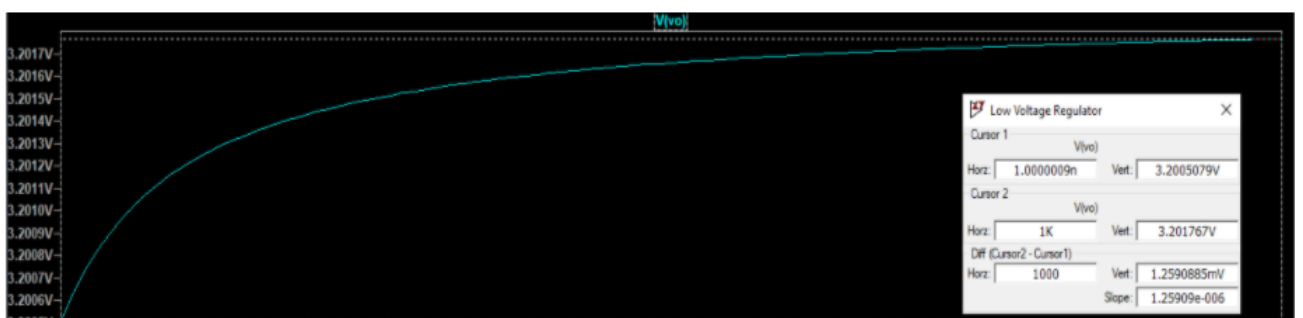

## 4. Results

- Voltage regulation calculation:

Configuration	Voltage regulation = $(-V_{(NL)} - V_{(FL)}) / V_{FL} \times 100\%$
Low voltage regulation	<b>0.0393%</b>
High voltage regulation	<b>0.6486%</b>

- Output voltage and current:

Configuration	Output current (mA)		Output voltage (V)	
	No-load	Full load	No-load	Full load
Low voltage regulation	2.91069 71	32.005079	3.201767	3.2005079
High voltage regulation	12.9658 92	141.70817	14.262482	14.170816