

To Study active filters using

Analog Electronics Lab Experiment -7

Submitted by : Jash Shah

BITS Id : 2018A8PS0507P

Lab Section: P5

Submitted to : Sambhavi Shukla, Teena Gakhar

Date : 13/3/21

1. Objective

To study the Active Filters using OP AMP (IC-741)

- 1) Half Wave Rectifier
- 2) Full Wave Rectifier
- 3) Positive Clipper
- 4) Negative Clipper

Report the following:


- 1) Circuit diagrams for all configurations.
- 2) Waveforms for all four configurations.

Assumptions:


- 1) Ideal behaviour of the OPAMP.
- 2) All the calculations to be done at 1kHz frequency.

2. High Wave Rectifier

1. Circuit Diagram:

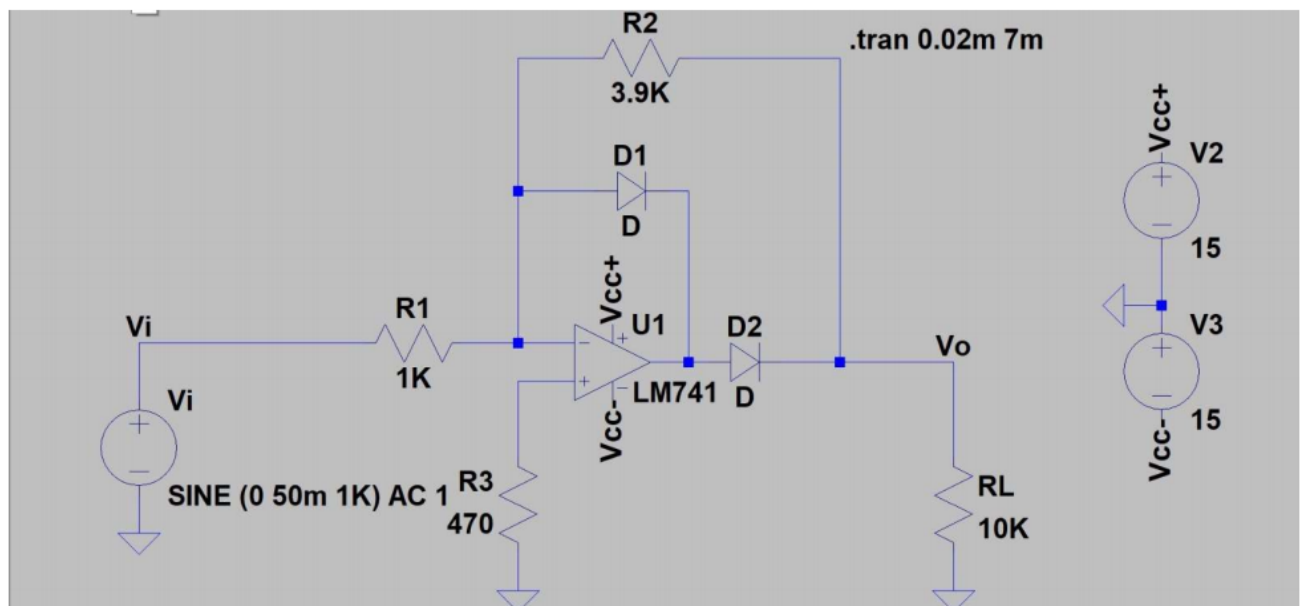

2. Resultant Curve and simulation result

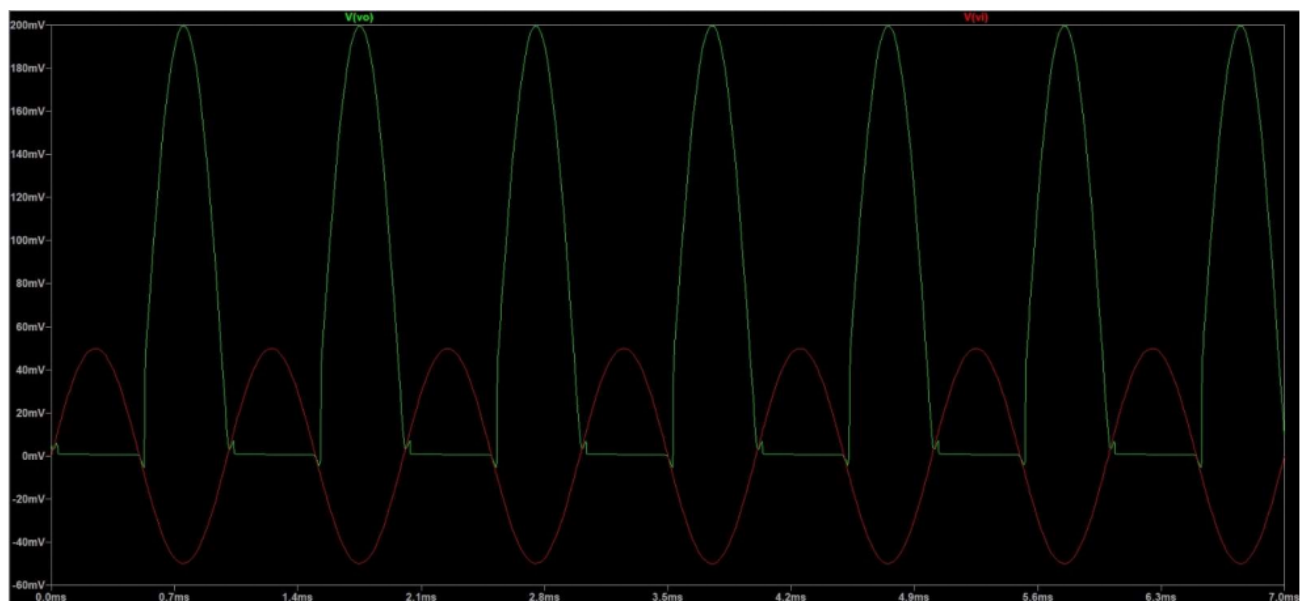


Simulated gain= $(V_o/V_i) = (-199.78/50) = -3.99$

3. Hand Calculations


Theoretical gain= $-(R2/R1) = -(3.9\text{k}/1\text{k}) = -3.9$

3. Full Wave Rectifier

1. Circuit Diagram:

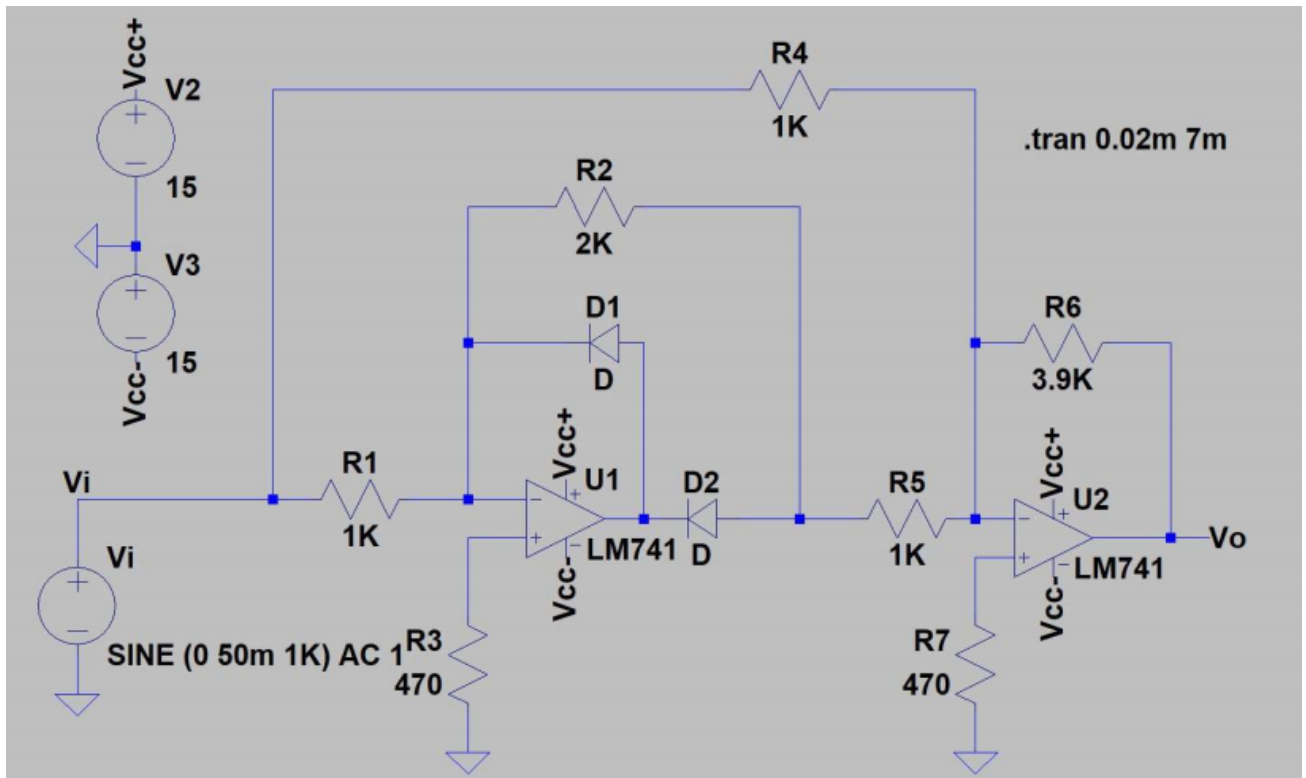

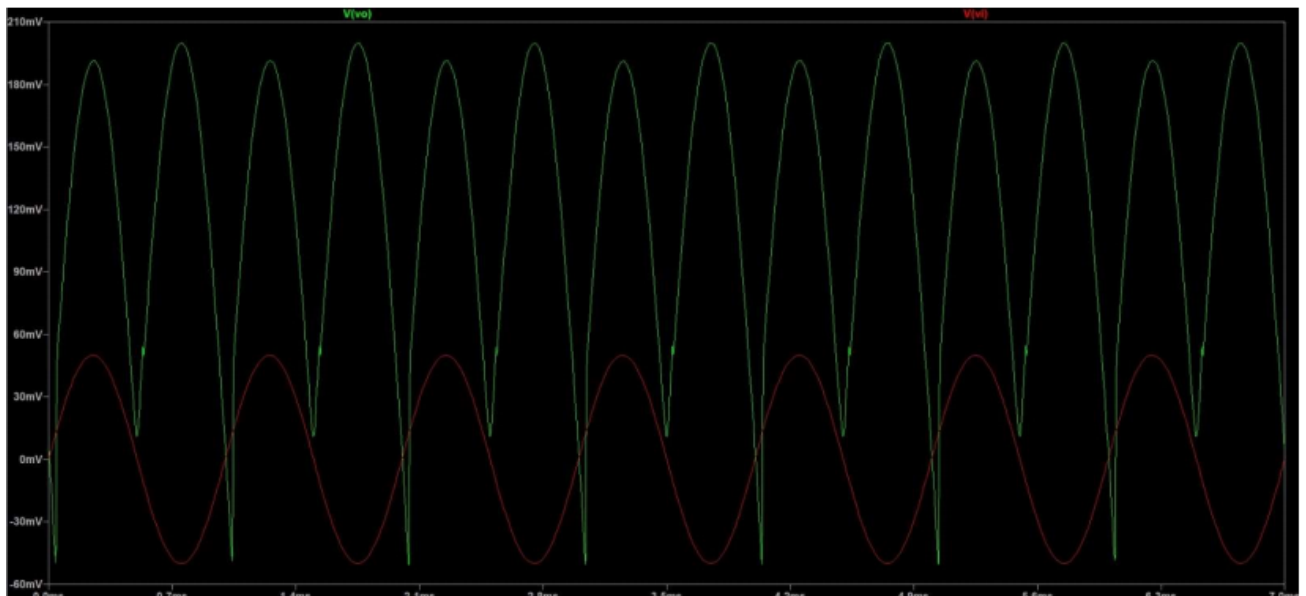2. Resultant analysis and simulated result



Simulated gain (for positive half cycle)= $(191.415\text{mV}/50\text{mV})= 3.82$


Simulated gain (for negative half cycle)= $-(199.9\text{mV}/50\text{mV})= -3.99$

3. Hand Calculations


Magnitude of Theoretical gain= $(R6/R4)= (3.9\text{k}/1\text{k})= 3.9$

4. Positive Clipper

1. Circuit Diagram:

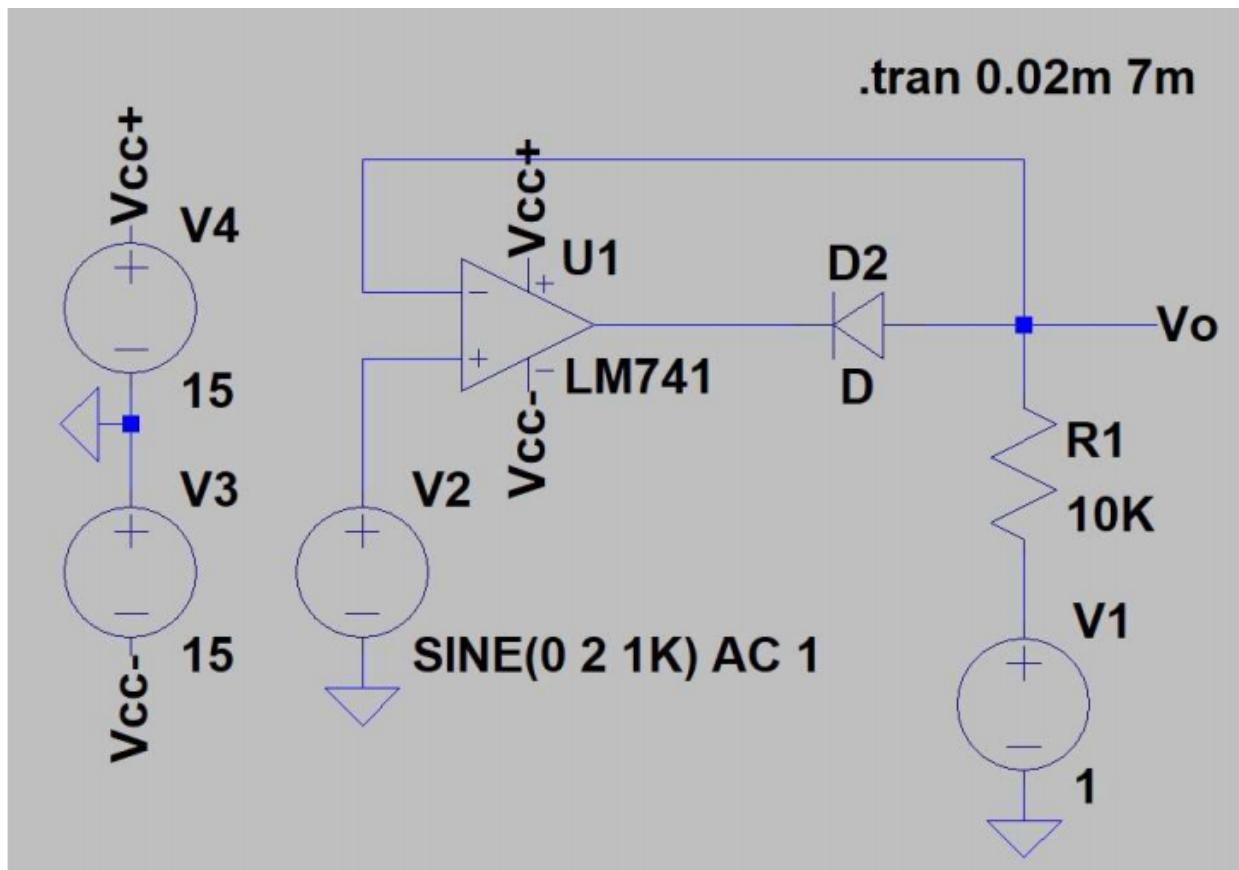


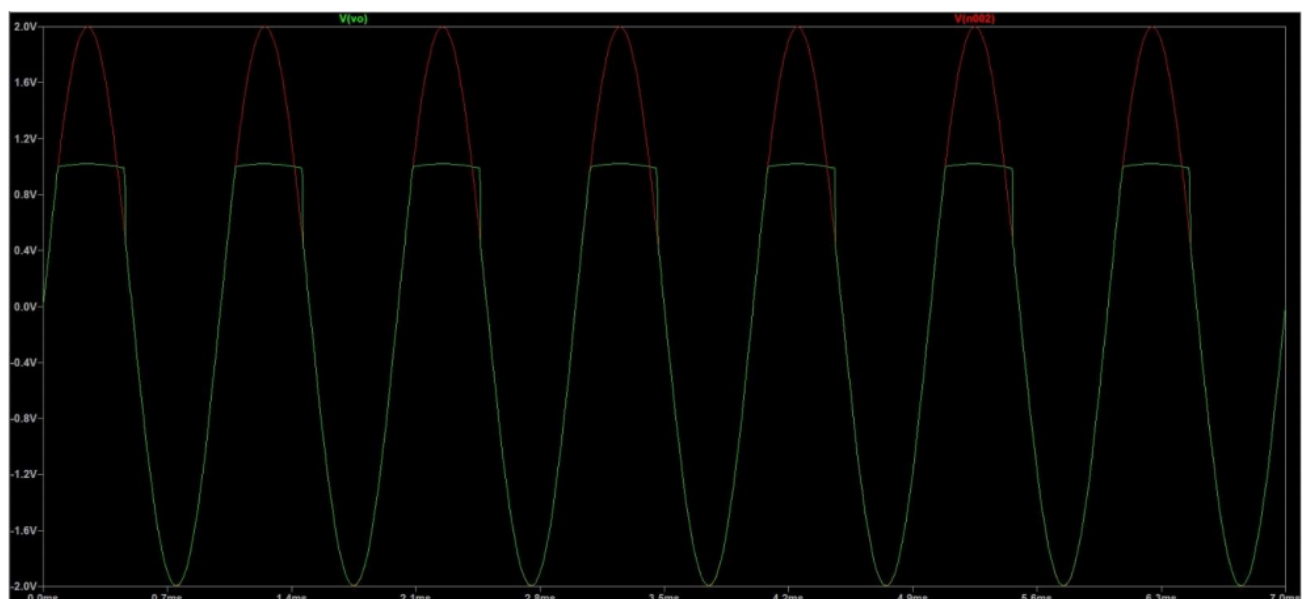2. Resultant analysis and simulation results



5. Negative Clipper

1. Circuit Diagram:

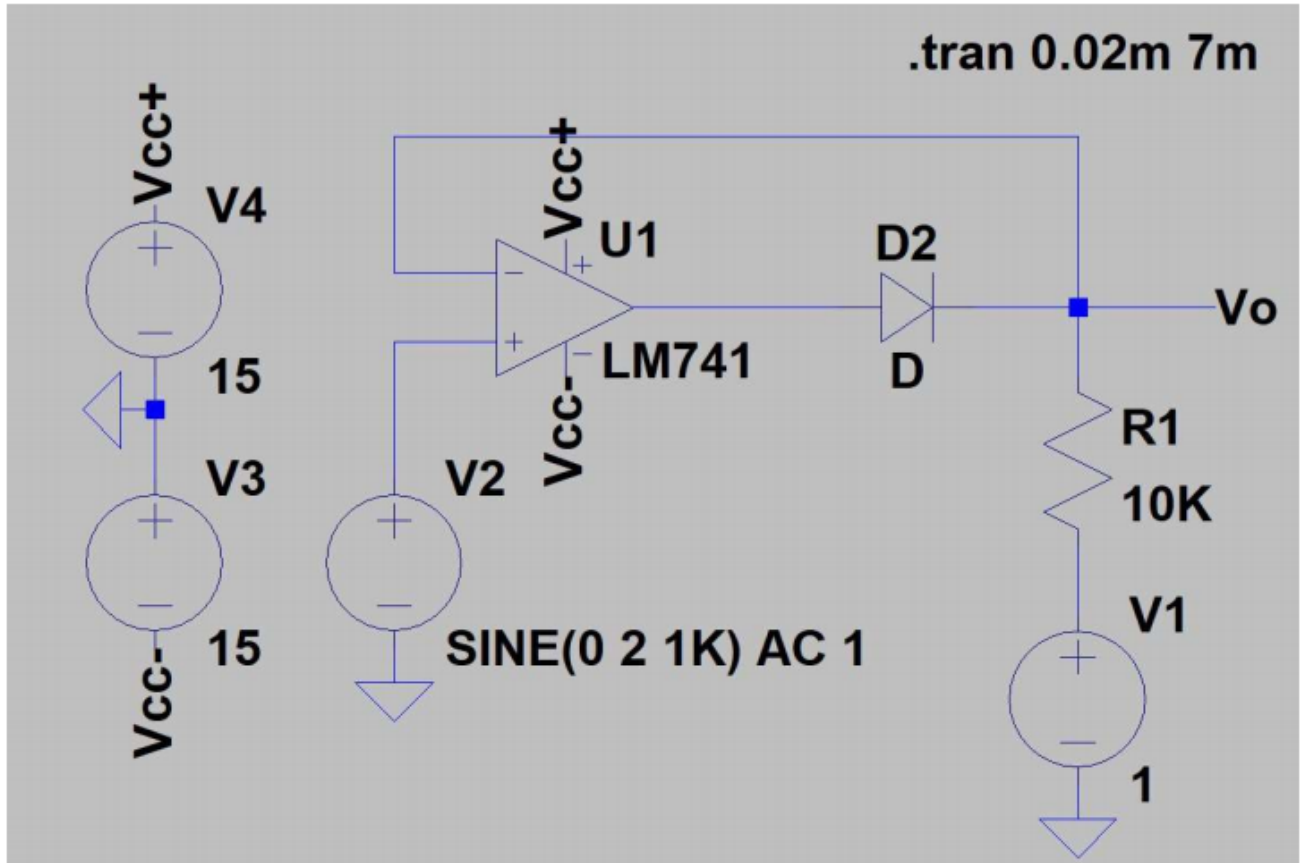

2. Resultant analysis and simulation results

