

# Oscillator Circuits

## Analog Electronics Lab Experiment -8

**Submitted by :** Jash Shah

**BITS Id :** 2018A8PS0507P

**Lab Section:** P5

**Submitted to :** Sambhavi Shukla, Teena Gakhar

**Date :** 20/3/21

---

### **1. Objective**

To study the sinusoidal and non-sinusoidal oscillators

1) RC phase shift oscillator

2) Wein Bridge Oscillator

Upload a single PDF file on Nalanda which includes


1) Circuit diagrams for all configurations.

2) Input and output waveforms


3) Compare your theoretical values with the practical ones.

## 2. RC Phase Shift Oscillator

### 1. Circuit Diagram:

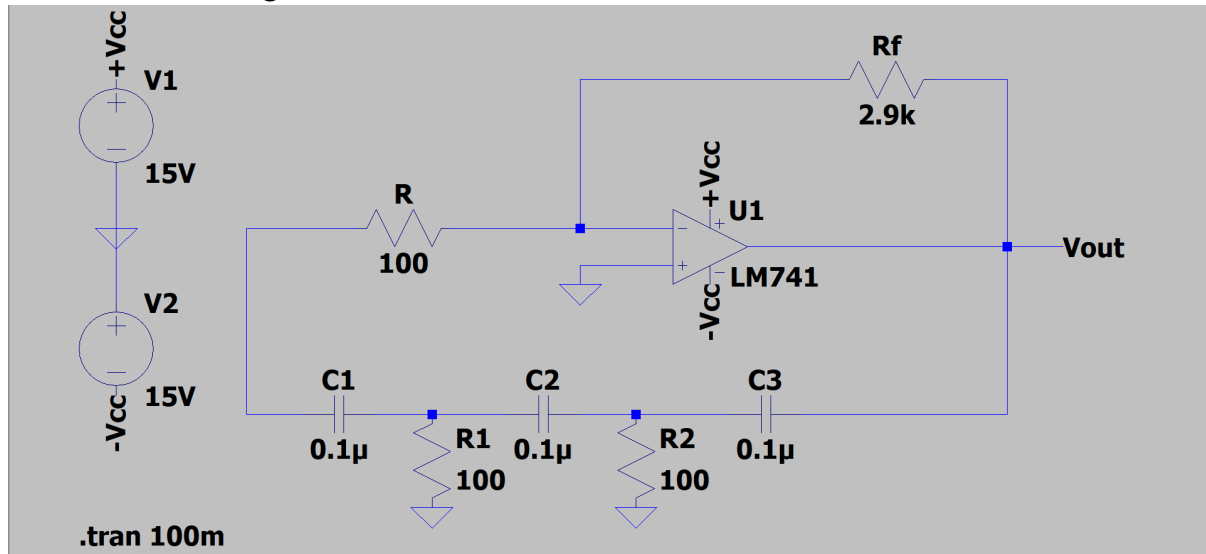
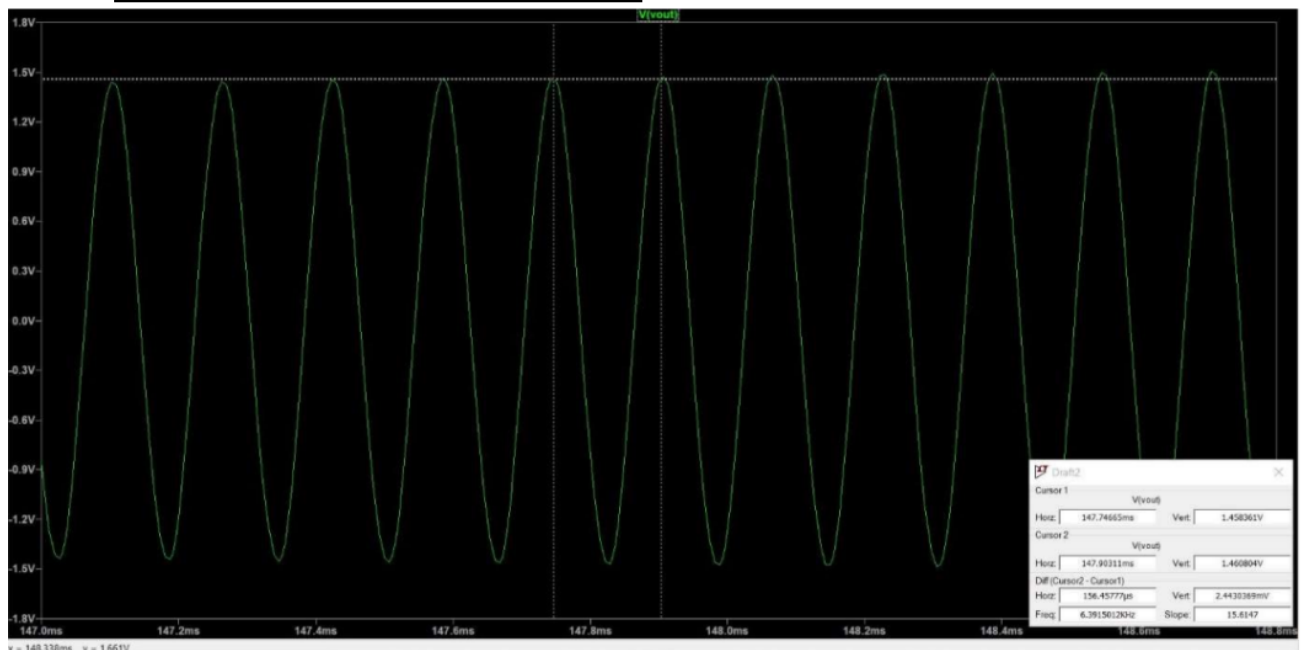
### 2. Resultant Curve and simulation result



Simulated gain = We get the practical value of, (at Rf = 2.9 k-ohm)


$$f_0 = 6.475 \text{ kHz}$$

### Hand Calculations

$$f_0 = 1/(2 \cdot \pi \cdot (6^{0.5}) \cdot R \cdot C) = 6.5 \text{ kHz}$$

### 3. Changing the value of C

$C \Rightarrow 2C$

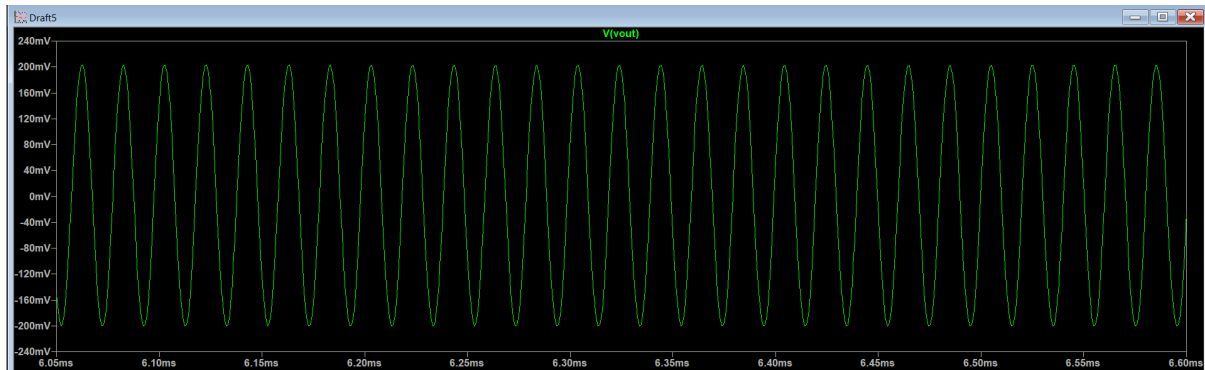

Practical frequency  $\Rightarrow 3.13$  kHz


Theoretical frequency  $\Rightarrow 3.25$  kHz

### 4. Changing the value of R


<u>Serial Number</u>	<u>Resistor</u>	<u>Frequency</u>
1	2	-
2	4	4.89
3	6	3.78
4	8	3.5
5	10	3.24

### 3. Wein Bridge Filter

#### 1. Circuit Diagram:

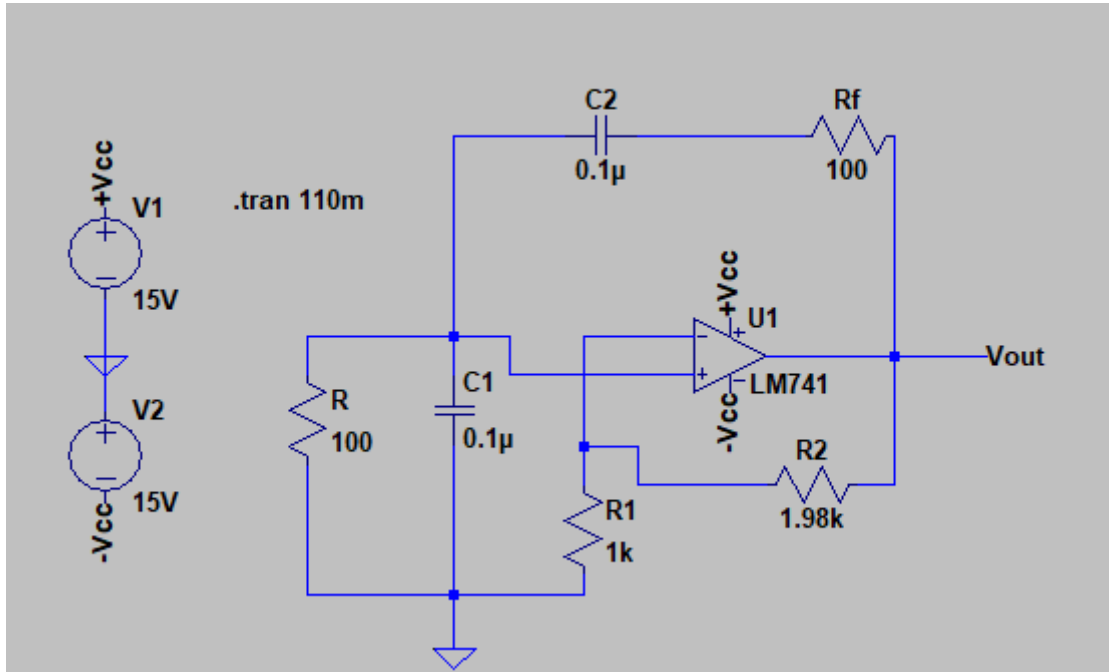
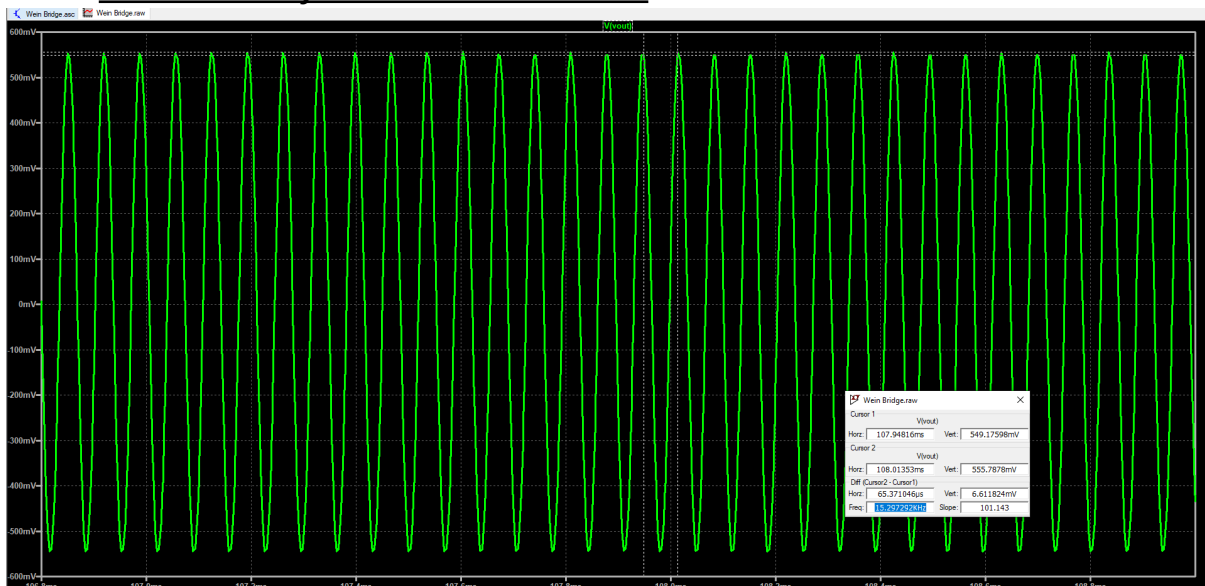
#### 2. Resultant analysis and simulated result



We get the practical value of, (at  $R_F = 1.98 \text{ k-ohm}$ )

$$f_0 = 15.297 \text{ kHz}$$

### Hand Calculations

The theoretical value of  $f_0$  is:

$$f_0 = 1/(2 \cdot \pi \cdot R \cdot C) = \mathbf{16 \text{ kHz}}$$

### 3. Changing the value of R

<u>Serial Number</u>	<u>Resistor</u>	<u>Frequency</u>
1	2	6.73
2	4	4.73
3	6	4.20
4	8	3.95
5	10	3.81