

Study of Instrumentation amplifier using OPAMP (IC-741)

Analog Electronics Lab Experiment -5

Submitted by : Jash Shah

BITS Id : 2018A8PS0507P

Lab Section: P5

Submitted to : Sambhavi Shukla, Teena Gakhar

Date : 20/2/21

1. Objective

To study the characteristics of an instrumentation feedback amplifier made using Operational Amplifier and verify the same using LTSpice simulation of IC 741:

Report the following:


- 1) Circuit diagrams after finding the DC null point.
- 2) Calculate the Voltage gain (A_v) for :
 - a) Common mode
 - b) Differential mode
- 3) Theoretical Voltage and simulated value of CMRR.

Assumptions:


- 1) Ideal behaviour of the OPAMP.
- 2) All the calculations to be done at 1kHz frequency.

2. DC Null Point

1. Circuit Diagram:

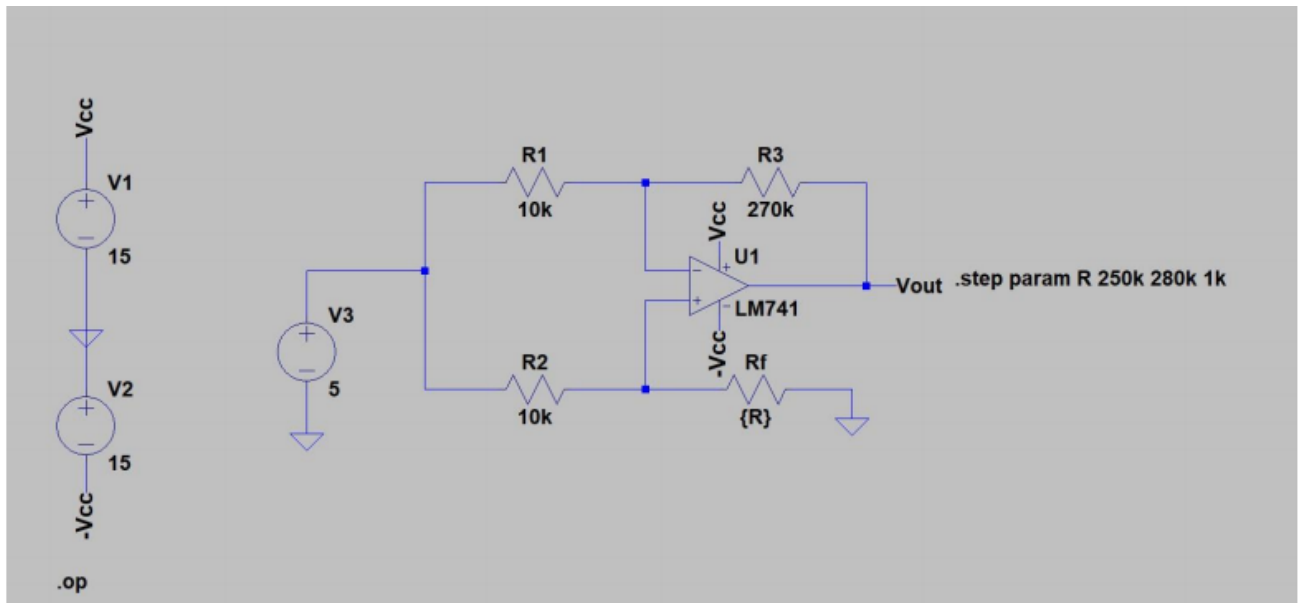

2. Resultant Curve and simulation result

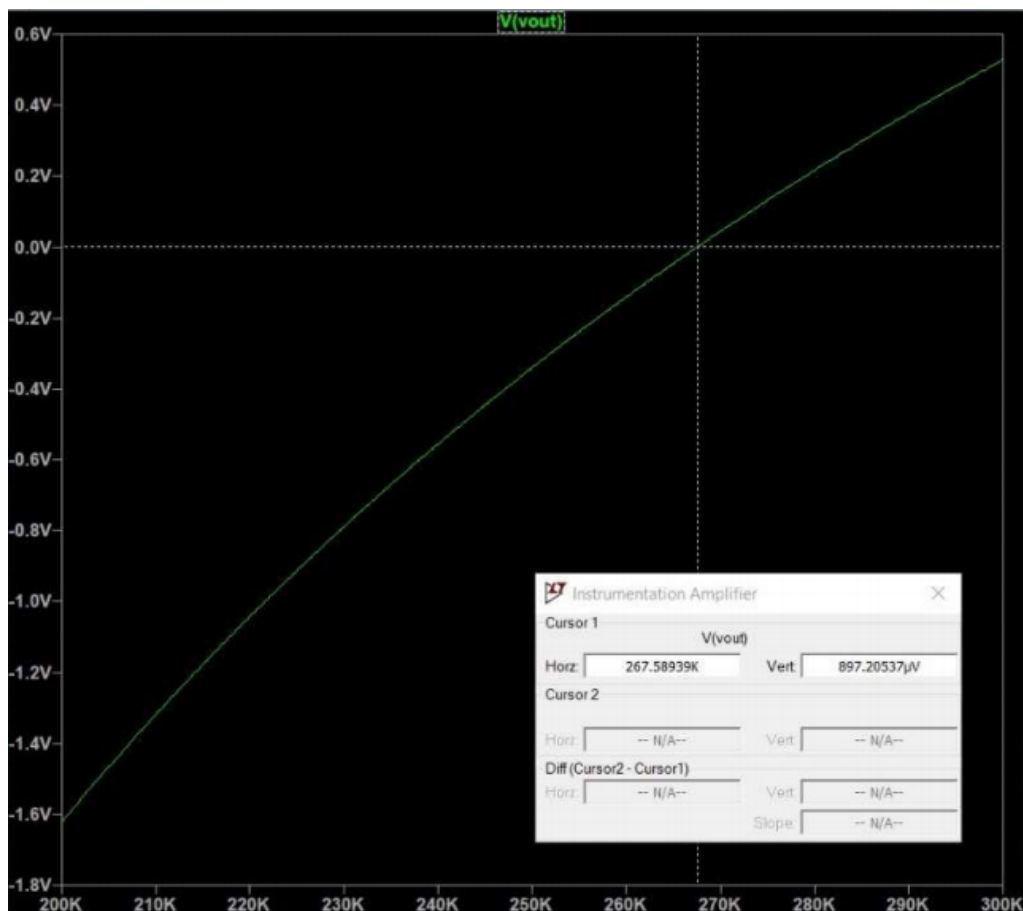


Simulated Value of R_f obtained = 267.58k ohm (approx.)

3. Hand Calculations

$$R1/R2 = Rf/R3 \text{ (for ideal Op-Amp)} \Rightarrow Rf = 270k \text{ ohm}$$

3. Common Mode Gain

1. Circuit Diagram:

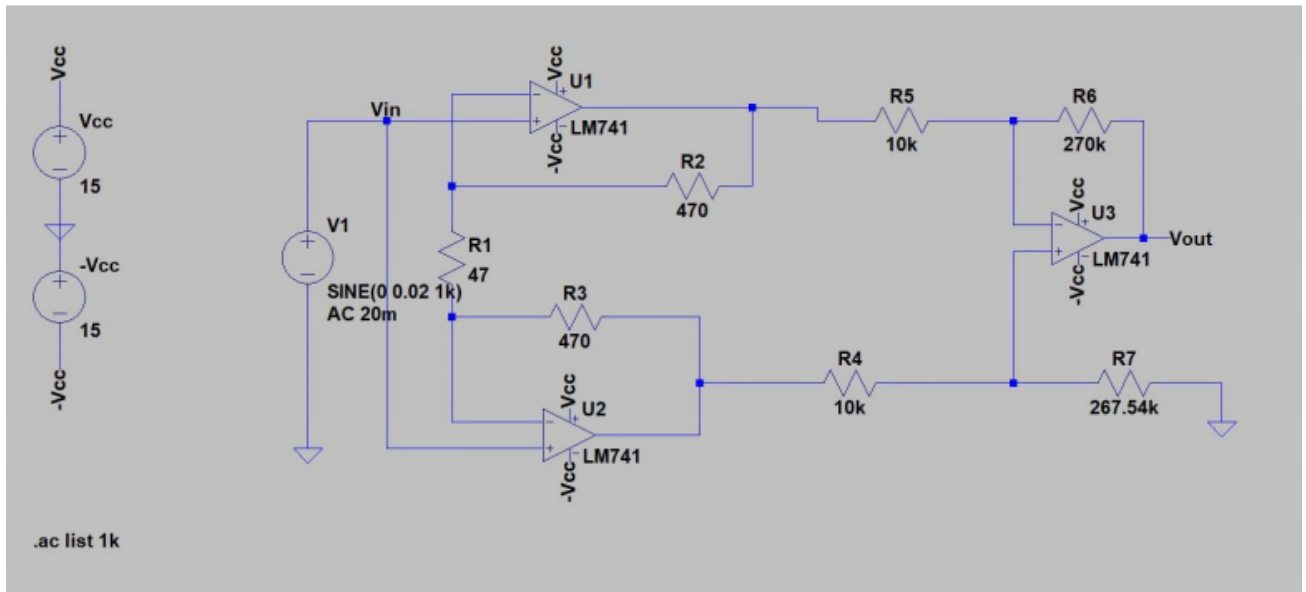

2. Resultant analysis and simulated result

--- AC Analysis ---				
frequency:	1000	Hz		
V(n001):	mag: 0.0192807	phase: -0.0446857°	voltage	
V(n003):	mag: 0.01928	phase: -0.0512225°	voltage	
V(vcc-):	mag: 0	phase: 0°	voltage	
V(vcc+):	mag: 0	phase: 0°	voltage	
V(vout):	mag: 0.000167435	phase: 157.439°	voltage	
V(b):	mag: 0.0200005	phase: -0.051356°	voltage	
V(a):	mag: 0.0200005	phase: -0.0513552°	voltage	
V(n002):	mag: 0.0200005	phase: -0.0512658°	voltage	
V(v1):	mag: 0.02	phase: 0°	voltage	
V(n004):	mag: 0.0200005	phase: -0.0512658°	voltage	
I(R7):	mag: 8.9088e-13	phase: -19.0189°	device_current	
I(R6):	mag: 6.69901e-11	phase: -88.5107°	device_current	
I(R5):	mag: 6.63868e-11	phase: -89.9513°	device_current	
I(R2):	mag: 7.19847e-08	phase: 179.77°	device_current	
I(R3):	mag: 7.20518e-08	phase: 179.945°	device_current	
I(R4):	mag: 7.20533e-08	phase: 179.949°	device_current	
I(R1):	mag: 7.19832e-08	phase: 179.766°	device_current	
I(V3):	mag: 1.33365e-10	phase: -89.2621°	device_current	
I(V1):	mag: 3.60453e-08	phase: 179.843°	device_current	
I(V2):	mag: 3.60099e-08	phase: -0.157328°	device_current	
Ix(u1:1):	mag: 4.87246e-12	phase: -107.116°	subckt_current	
Ix(u1:2):	mag: 4.88392e-12	phase: 72.4518°	subckt_current	
Ix(u1:99):	mag: 3.60229e-08	phase: 179.766°	subckt_current	
Ix(u1:50):	mag: 3.59603e-08	phase: 179.766°	subckt_current	
Ix(u1:28):	mag: 7.19832e-08	phase: -0.233705°	subckt_current	
Ix(u2:1):	mag: 6.66826e-11	phase: 90.7379°	subckt_current	
Ix(u2:2):	mag: 6.66832e-11	phase: -89.2278°	subckt_current	
Ix(u2:99):	mag: 3.6006e-08	phase: -0.282833°	subckt_current	
Ix(u2:50):	mag: 3.5979e-08	phase: -0.282833°	subckt_current	
Ix(u2:28):	mag: 7.1985e-08	phase: 179.717°	subckt_current	
Ix(u3:1):	mag: 6.66827e-11	phase: 90.738°	subckt_current	
Ix(u3:2):	mag: 6.66832e-11	phase: -89.2277°	subckt_current	
Ix(u3:99):	mag: 3.60623e-08	phase: -0.108177°	subckt_current	
Ix(u3:50):	mag: 3.59913e-08	phase: -0.108177°	subckt_current	
Ix(u3:28):	mag: 7.20537e-08	phase: 179.892°	subckt_current	


Simulated Value of A_{cm} obtained = $V_o/V_{in} = 0.00837$ (-41.54dB)

3. Hand Calculations

$$A_{cm} = 0$$

4. Differential mode gain

1. Circuit Diagram:

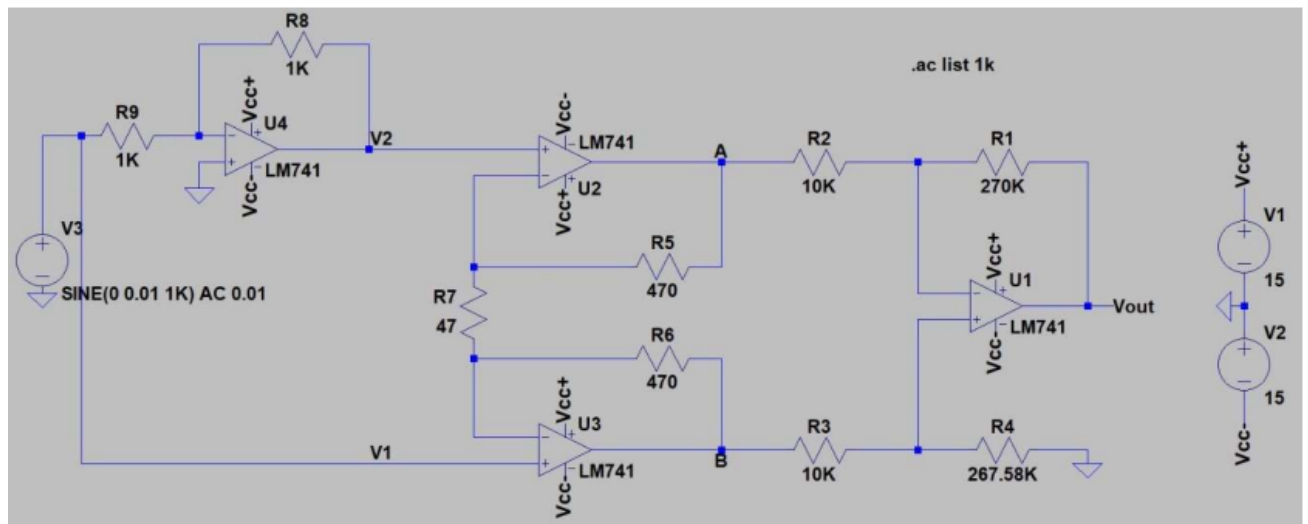

2. Resultant analysis and simulation results

--- AC Analysis ---				
frequency:	1000	Hz		
V(n002):	mag: 0.202268	phase: -5.02225°	voltage	
V(n004):	mag: 0.202314	phase: -1.81952°	voltage	
V(vcc-):	mag: 0	phase: 0°	voltage	
V(vcc+):	mag: 0	phase: 0°	voltage	
V(vout):	mag: 11.3257	phase: -3.42458°	voltage	
V(b):	mag: 0.209888	phase: -1.7101°	voltage	
V(a):	mag: 0.209888	phase: 178.282°	voltage	
V(n003):	mag: 0.00999483	phase: 178.199°	voltage	
V(v2):	mag: 0.00999987	phase: 179.864°	voltage	
V(n005):	mag: 0.00999455	phase: -1.62725°	voltage	
V(v1):	mag: 0.01	phase: 0°	voltage	
V(n001):	mag: 1.1816e-05	phase: 89.6166°	voltage	
I(R9):	mag: 9.99993e-06	phase: 179.932°	device_current	
I(R8):	mag: 9.99993e-06	phase: 179.932°	device_current	
I(R7):	mag: 0.000425306	phase: -1.71411°	device_current	
I(R6):	mag: 0.000425306	phase: -1.71425°	device_current	
I(R5):	mag: 0.000425306	phase: 178.286°	device_current	
I(R2):	mag: 4.11985e-05	phase: -3.33976°	device_current	
I(R3):	mag: 7.58442e-07	phase: -178.79°	device_current	
I(R4):	mag: 7.56088e-07	phase: 178.18°	device_current	
I(R1):	mag: 4.11983e-05	phase: -3.39553°	device_current	
I(V3):	mag: 9.99996e-06	phase: 179.938°	device_current	
I(V1):	mag: 0.000128319	phase: -1.72878°	device_current	
I(V2):	mag: 0.00011908	phase: -1.8693°	device_current	
Ix(u1:1):	mag: 4.01028e-08	phase: 86.331°	subckt_current	
Ix(u1:2):	mag: 4.01028e-08	phase: -93.6684°	subckt_current	
Ix(u1:99):	mag: 2.00714e-05	phase: -3.39553°	subckt_current	
Ix(u1:50):	mag: 2.11269e-05	phase: -3.39553°	subckt_current	
Ix(u1:28):	mag: 4.11983e-05	phase: 176.604°	subckt_current	
Ix(u2:1):	mag: 1.03156e-09	phase: -91.9873°	subckt_current	
Ix(u2:2):	mag: 1.03156e-09	phase: 88.0138°	subckt_current	
Ix(u2:99):	mag: 0.000300315	phase: 178.142°	subckt_current	
Ix(u2:50):	mag: 0.000166174	phase: 178.142°	subckt_current	
Ix(u2:28):	mag: 0.000466489	phase: -1.85779°	subckt_current	
Ix(u3:1):	mag: 1.00805e-09	phase: 88.061°	subckt_current	
Ix(u3:2):	mag: 1.00805e-09	phase: -91.9379°	subckt_current	
Ix(u3:99):	mag: 0.000156966	phase: -1.70904°	subckt_current	
Ix(u3:50):	mag: 0.000269098	phase: -1.70904°	subckt_current	

V1 = 10 mV, V2 = -10mV, Vi = 20mV

Vout = 11.3257

Adm = Vo/Vi = 566.285 (55.06 dB)

3. Hand Calculations

$$A_{dm} = (R_1/R_2) \times (1 + 2 \cdot R_5/R_7) = 567 \text{ (55.07 dB)}$$

5. CMRR

The Common Mode Rejection Ratio is defined as the ratio of differential-mode gain to the common-mode gain.

1. Simulated value

$$\text{CMRR} = A_{dm} / A_{cm} = 67616.12 \text{ (96.6 dB)}$$

2. Hand Calculations

$$A_{dm} = 567 \text{ and } A_{cm} = 0$$

$$\Rightarrow \text{CMRR} = \text{Infinite}$$