

Study of different modes of common collector amplifier

Analog Electronics Lab Experiment -2

Submitted by : Jash Shah

BITS Id : 2018A8PS0507P

Lab Section: P5

Submitted to : Sambhavi Shukla, Teena Gakhar

Date : 3/2/21

1. Objective

To study the common-collector amplifier, Darlington mode transistors, and bootstrapped emitter follower. Design the circuit on LT-Spice and calculate the following parameters

- 1) DC Bias Point
- 2) Input Resistance
- 3) Output Resistance
- 4) Voltage Gain
- 5) Show the waveforms for input and output voltages

Given Information:

Load Resistance = 5.6k Ohms,

Input series resistance = 10k Ohms,

Coupling and Bypass Capacitor = 10uF

Emitter Resistance = 3.9k Ohms


Potential Divider consists of : 39k Ohms (Lower arm) and 10k + R Ohms (Upper arm)

Components provided : BJT, Capacitor, Resistor, Voltage Source AC and DC. wires


Assumptions: Assuming that the DC bias point i.e. $V_c - V_e = V_{bias}/2 = 5V$

2. Schematic Diagram

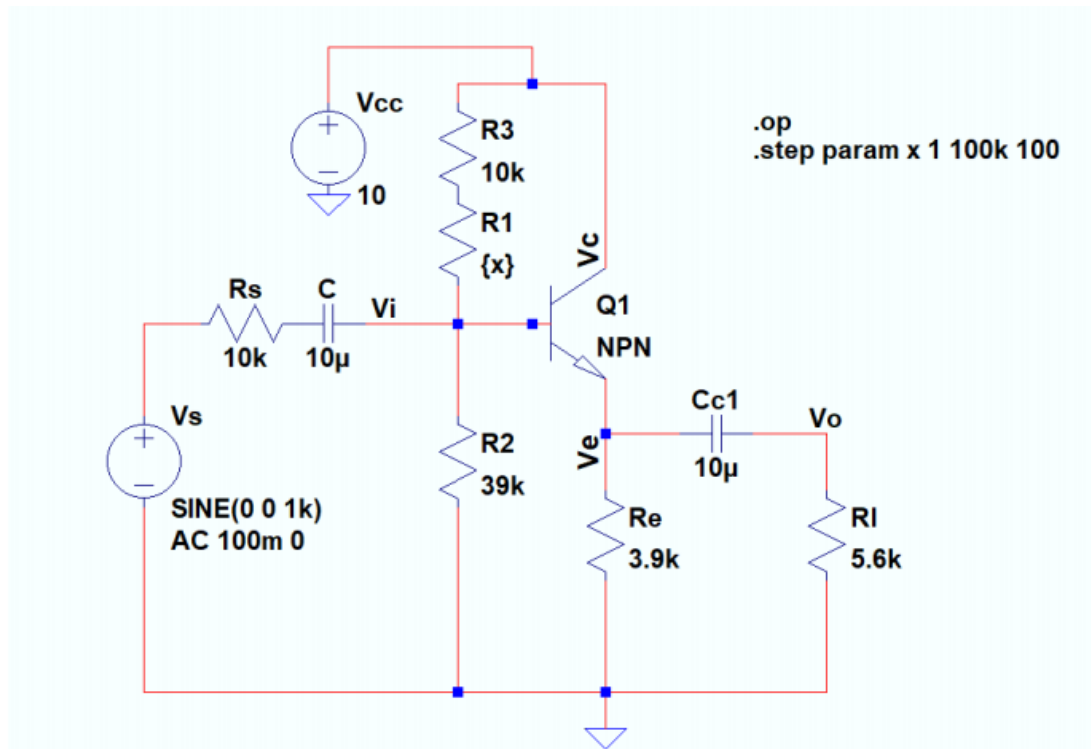
A. Common Collector amplifier Schematic :



B. Darlington mode transistor Schematic:

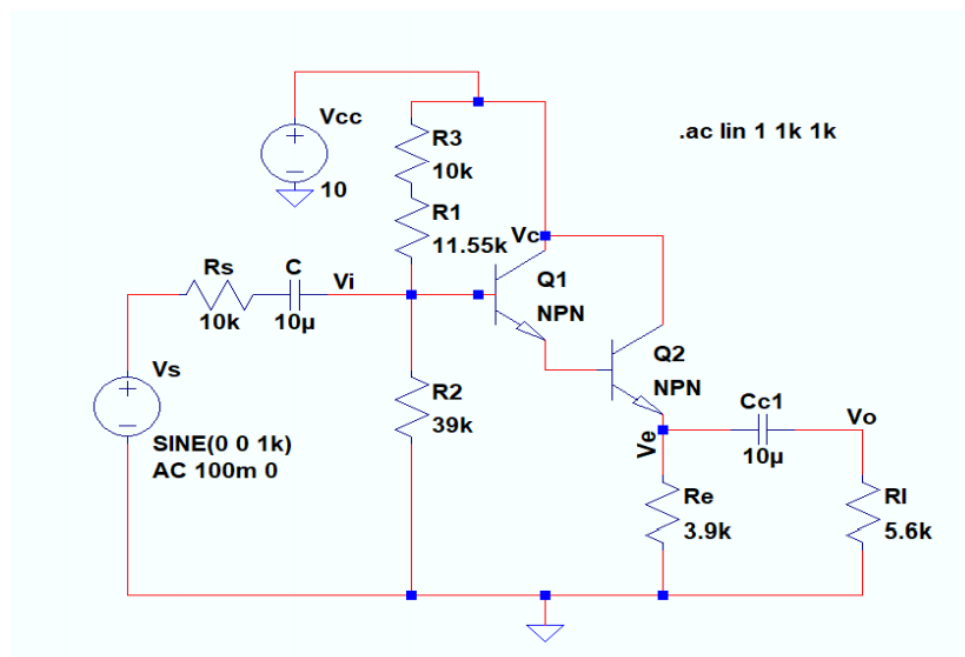


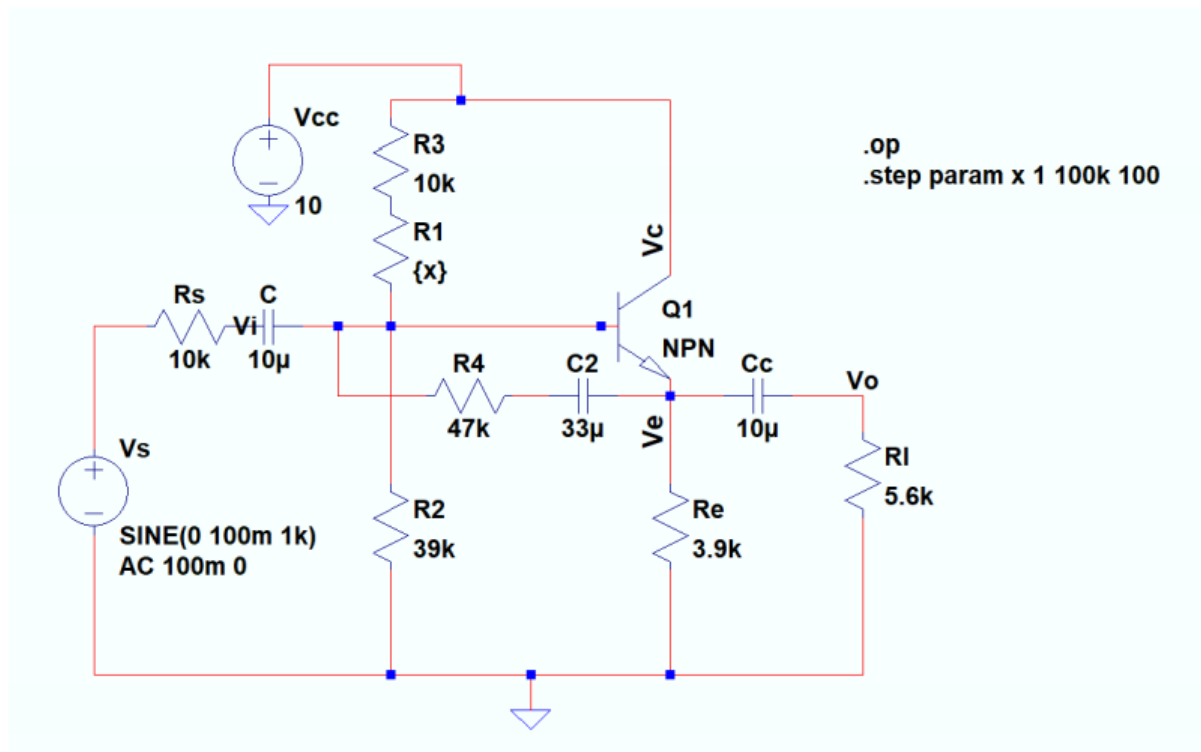
C. Bootstrapped emitter follower Schematic:



3. DC Bias Point Calculation

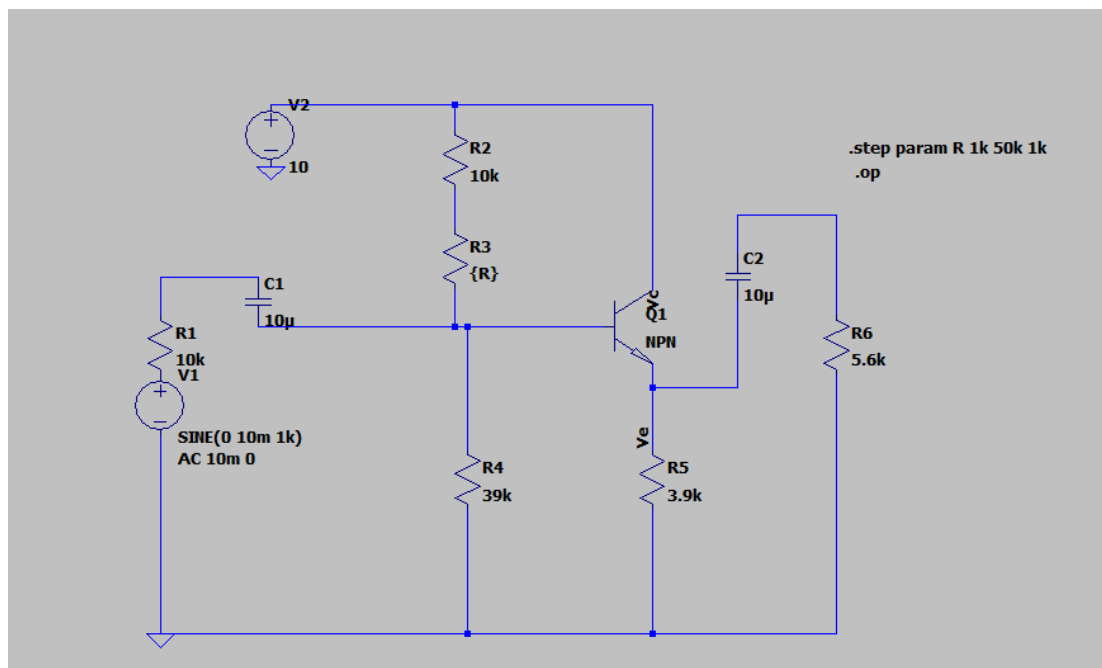A. Common Collector amplifier Schematic :




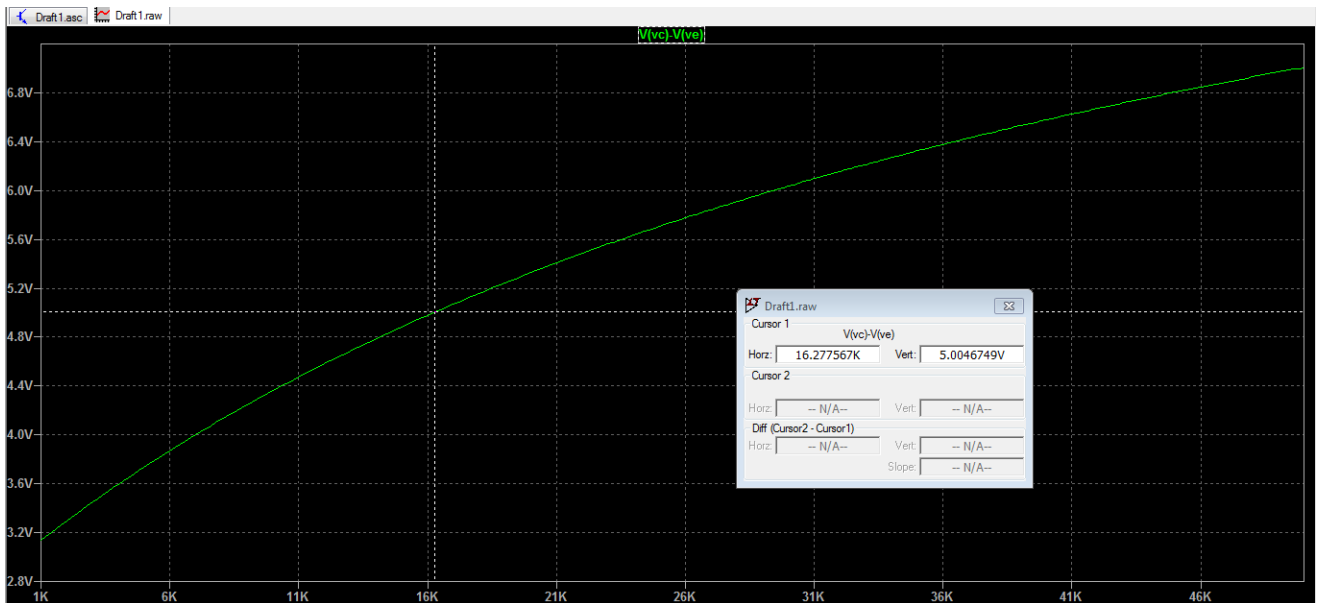


The value of $R_3 = 16.240304\text{K}\Omega$

So, the value of total resistance in upper arm = $10\text{K} + 16.240304\text{K} = 26.24\text{K}$


B. Darlington Pair :

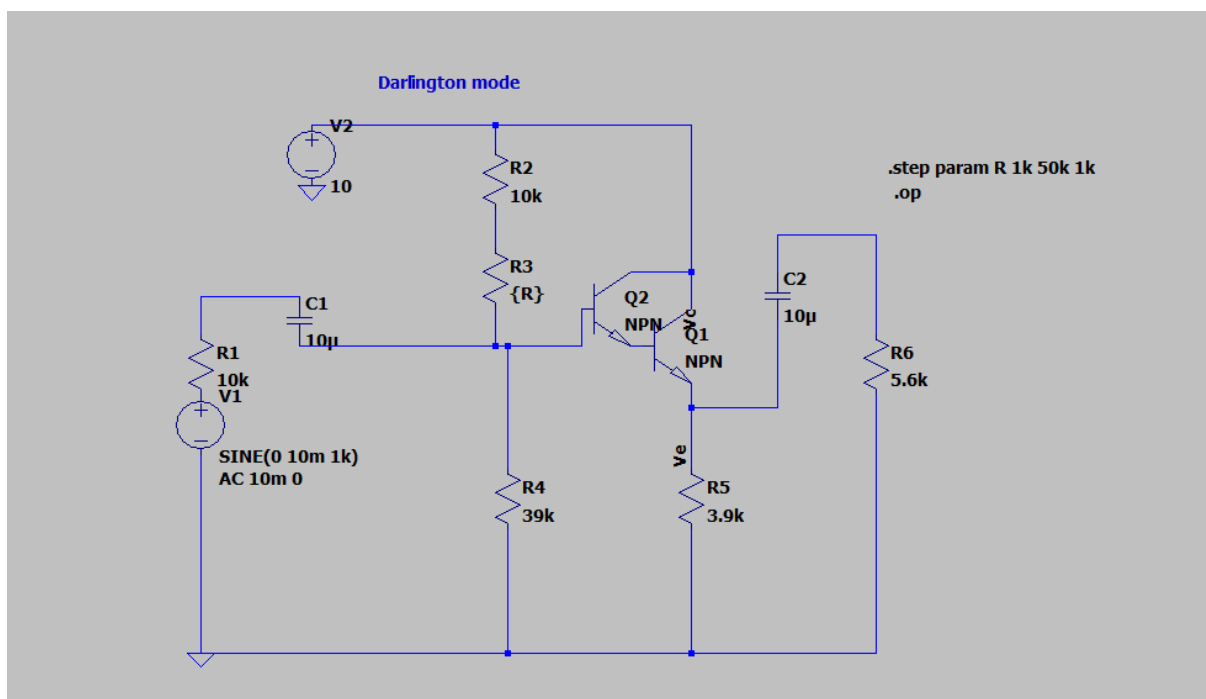


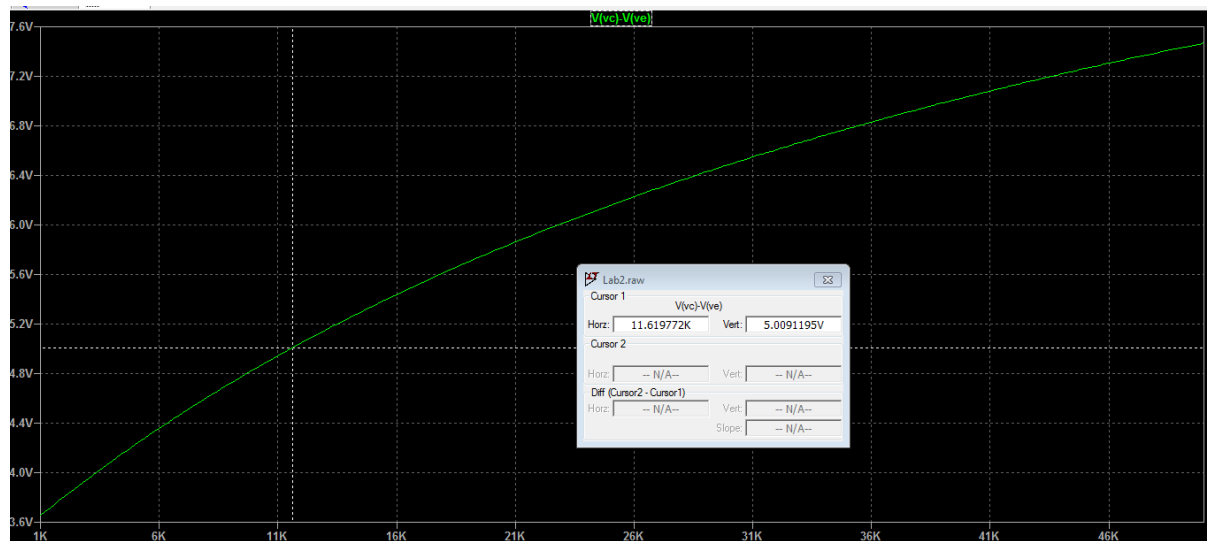

Here the value of R3 is 11.545247K
 So, total resistance in upper arm is 21.545247K

C. Bootstrapped configuration :

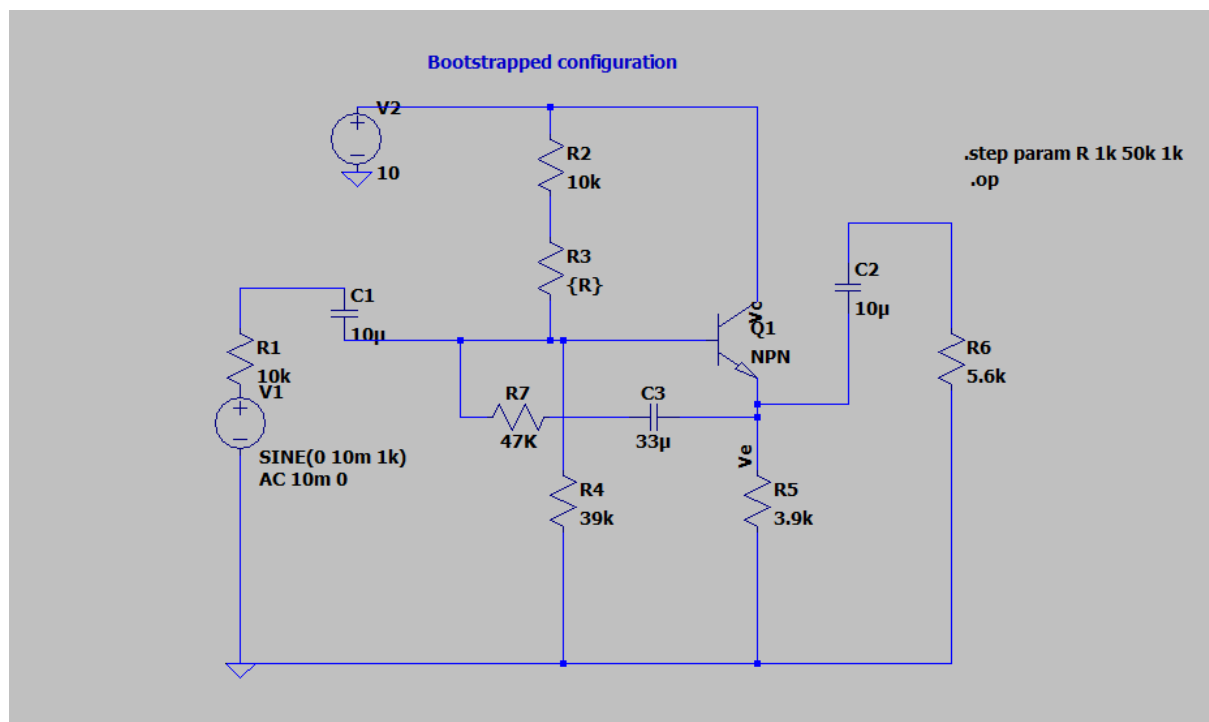

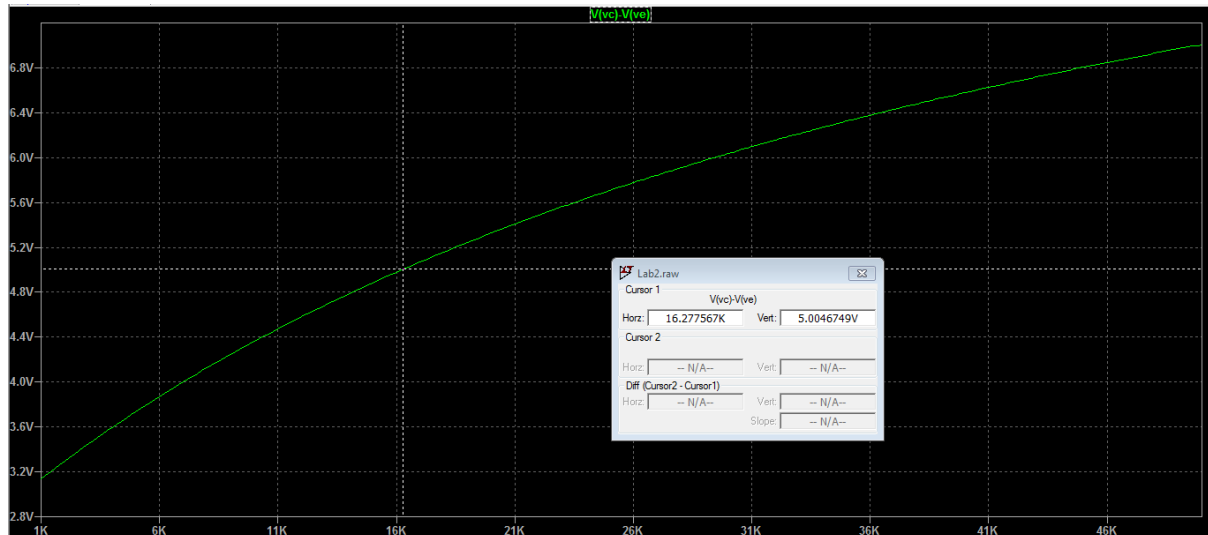


Value of R3 = 16.277567K

So, total resistance in upper arm = 26.28 KOHms

4. Rin and Gain Calculation

For this, I used AC analysis at 1k Frequency

A. For Common Collector Configuration

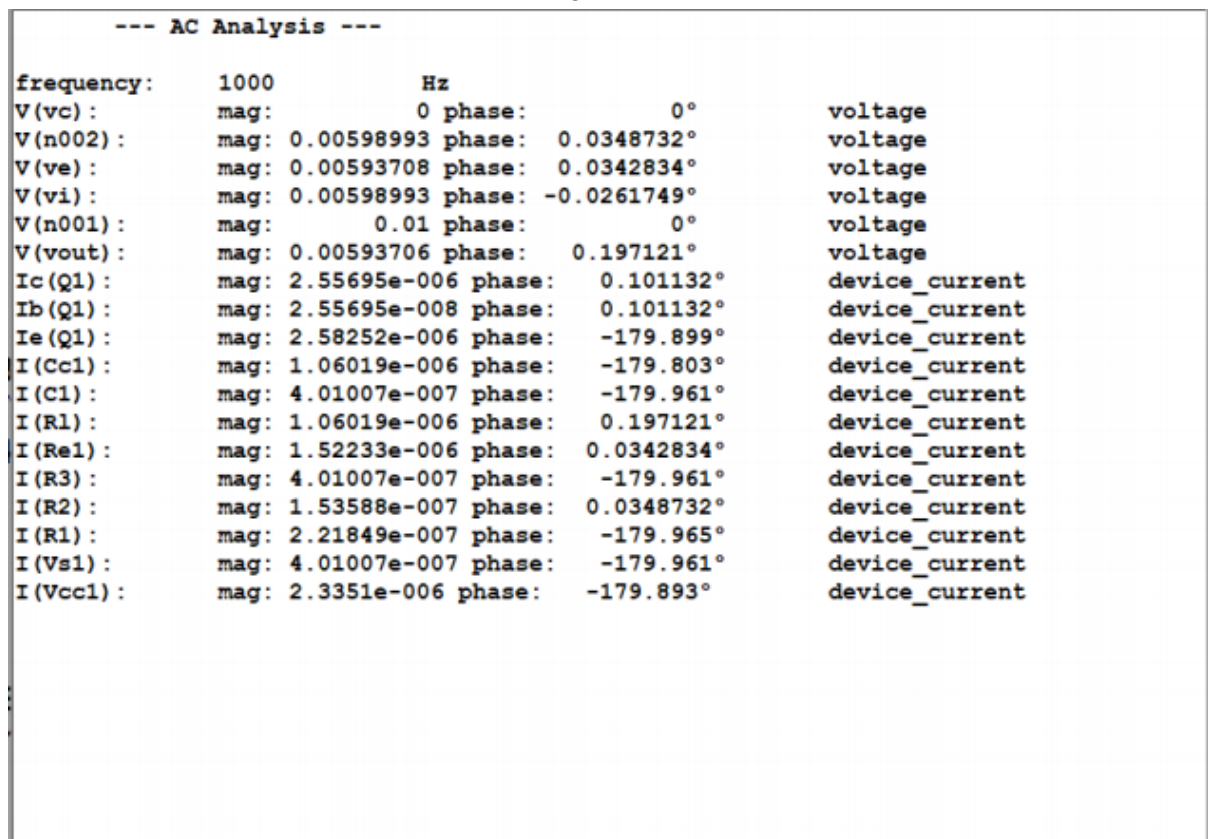

$$A_v = 0.00593/0.00598 = 0.991$$

$$R_{in} = 0.00598/0.4\mu A = 14.95\text{kohms}$$

B. Darlington Pair

```

--- AC Analysis ---

frequency:      1000      Hz
V(vc):          mag:      0 phase:      0°      voltage
V(n002):        mag: 0.0062586 phase: 0.0341002° voltage
V(n003):        mag: 0.00620457 phase: 0.0335281° voltage
V(vi):          mag: 0.00625861 phase: -0.0204126° voltage
V(n001):        mag:      0.01 phase:      0°      voltage
V(ve):          mag: 0.00615054 phase: 0.032946° voltage
V(vout):        mag: 0.00615052 phase: 0.195783° voltage
Ic(Q2):         mag: 2.64888e-006 phase: 0.0997948° device_current
Ib(Q2):         mag: 2.64888e-008 phase: 0.0997948° device_current
Ie(Q2):         mag: 2.67537e-006 phase: -179.9° device_current
Ic(Q1):         mag: 2.62265e-008 phase: 0.0997948° device_current
Ib(Q1):         mag: 2.62271e-010 phase: 0.0997932° device_current
Ie(Q1):         mag: 2.64888e-008 phase: -179.9° device_current
I(Cc1):         mag: 1.09831e-006 phase: -179.804° device_current
I(C1):          mag: 3.7414e-007 phase: -179.966° device_current
I(R1):          mag: 1.09831e-006 phase: 0.195783° device_current
I(Re1):         mag: 1.57706e-006 phase: 0.032946° device_current
I(R3):          mag: 3.7414e-007 phase: -179.966° device_current
I(R2):          mag: 1.33162e-007 phase: 0.0341002° device_current
I(R1):          mag: 2.40715e-007 phase: -179.966° device_current
I(Vs1):         mag: 3.7414e-007 phase: -179.966° device_current
I(Vcc1):        mag: 2.43439e-006 phase: -179.894° device_current

```

$$A_v = 0.00615052 / 0.00625861 = 0.9827$$

$$R_{in} = 0.00625861 / 0.3741 \mu A = 16.7 \text{ kohms}$$

C. Bootstrapped mode

```

--- AC Analysis ---

frequency:      1000      Hz
V(vc):          mag:      0 phase:      0°      voltage
V(n002):        mag: 0.00598327 phase: 0.0348556° voltage
V(ve):          mag: 0.00593051 phase: 0.0342661° voltage
V(vi):          mag: 0.00598328 phase: -0.0263619° voltage
V(n001):        mag:      0.01 phase:      0°      voltage
V(vout):        mag: 0.00593048 phase: 0.197103° voltage
V(n003):        mag: 0.00593051 phase: 0.0342138° voltage
Ic(Q1):         mag: 2.553e-006 phase: 0.101112° device_current
Ib(Q1):         mag: 2.553e-008 phase: 0.101112° device_current
Ie(Q1):         mag: 2.57853e-006 phase: -179.899° device_current
I(C3):          mag: 1.12268e-009 phase: -179.893° device_current
I(Cc1):         mag: 1.05901e-006 phase: -179.803° device_current
I(C1):          mag: 4.01673e-007 phase: -179.961° device_current
I(R4):          mag: 1.12268e-009 phase: 0.106992° device_current
I(R1):          mag: 1.05901e-006 phase: 0.197103° device_current
I(Re1):         mag: 1.52064e-006 phase: 0.0342661° device_current
I(R3):          mag: 4.01673e-007 phase: -179.961° device_current
I(R2):          mag: 1.53417e-007 phase: 0.0348556° device_current
I(R1):          mag: 2.21603e-007 phase: -179.965° device_current
I(Vs1):         mag: 4.01673e-007 phase: -179.961° device_current
I(Vcc1):        mag: 2.3314e-006 phase: -179.893° device_current


```

$$A_v = 0.00593048 / 0.00598328 = 0.9911$$

$$R_{in} = 0.00598328 / 0.40167 \mu A = 14.76 \text{ kohms}$$


5. Rout Calculations

a. For Common Collector Configuration

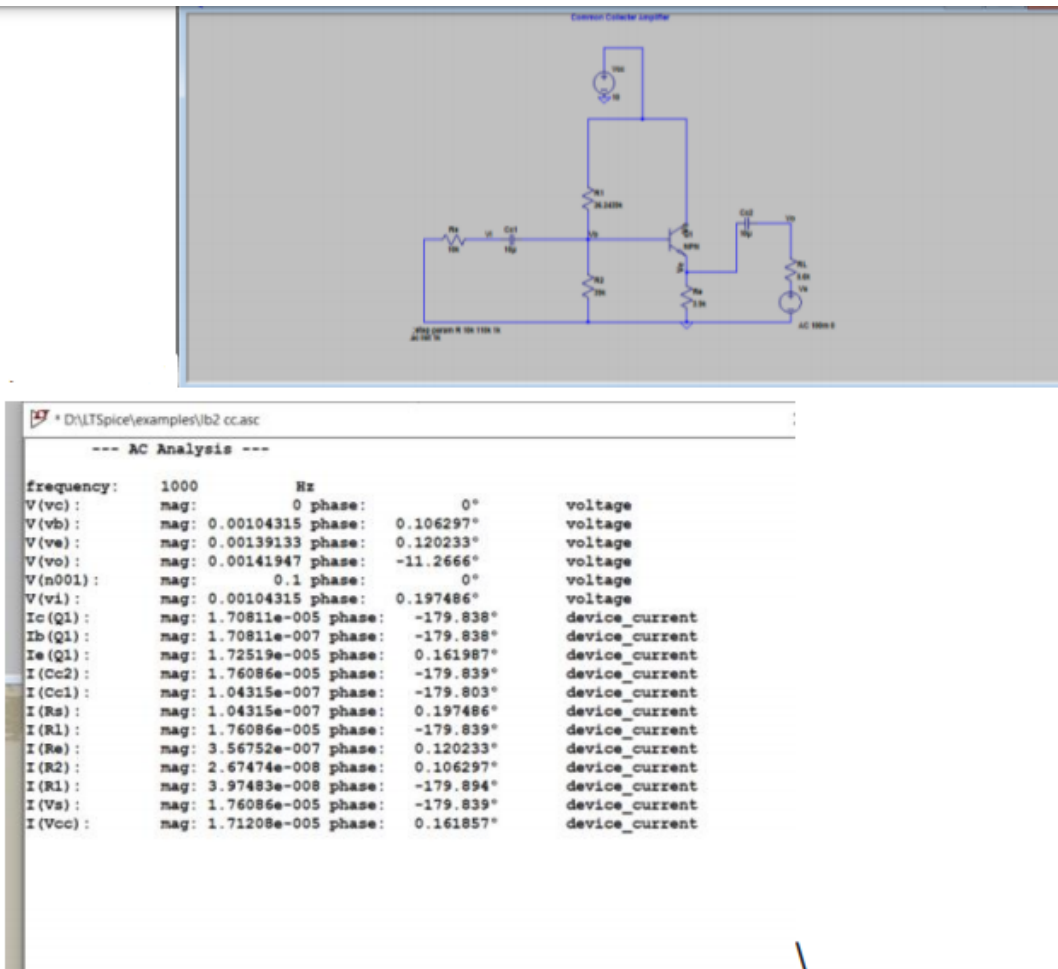

$R_{out}=80.612\Omega$

b. Darlington Pair

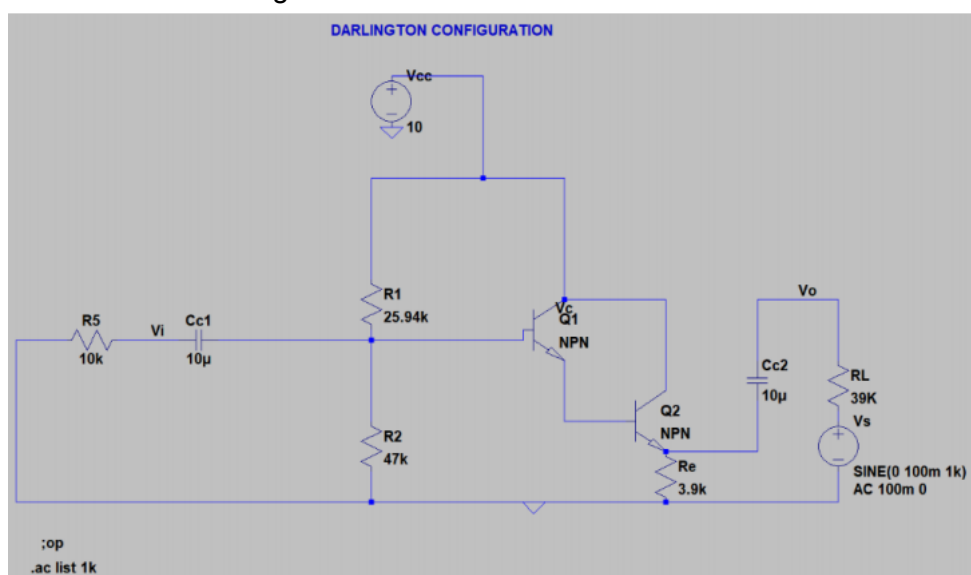


```

--- AC Analysis ---
frequency:      1000      Hz
V(vc):          mag:      0 phase:      0°      voltage
V(n001):        mag: 1.55473e-006 phase: -0.0336875° voltage
V(n004):        mag: 0.00010383 phase: 0.022513° voltage
V(vo):          mag: 0.00011547 phase: -21.4137° voltage
V(n003):        mag:      0.1 phase:      0°      voltage
V(vi):          mag: 1.55472e-006 phase: 0.0575015° voltage
V(n002):        mag: 5.26926e-005 phase: 0.0216839° voltage
Ic(Q1):         mag: 2.48487e-008 phase: -179.977° device_current
Ib(Q1):         mag: 2.48487e-010 phase: -179.977° device_current
Ie(Q1):         mag: 2.50972e-008 phase: 0.0233673° device_current
Ic(Q2):         mag: 2.50972e-006 phase: -179.977° device_current
Ib(Q2):         mag: 2.50972e-008 phase: -179.977° device_current
Ie(Q2):         mag: 2.53482e-006 phase: 0.0233673° device_current
I(Cc2):         mag: 2.56144e-006 phase: 0.0233584° device_current
I(Cc1):         mag: 1.55472e-010 phase: 0.0575015° device_current
I(R5):          mag: 1.55472e-010 phase: 0.0575015° device_current
I(R1):          mag: 2.56144e-006 phase: -179.977° device_current
I(Re):          mag: 2.66232e-008 phase: 0.022513° device_current
I(R2):          mag: 3.30793e-011 phase: -0.0336875° device_current
I(R1):          mag: 5.99355e-011 phase: 179.966° device_current
I(Vs):          mag: 2.56144e-006 phase: -179.977° device_current
I(Vcc):         mag: 2.53463e-006 phase: 0.0233659° device_current

```

Rout= 45.08Ω

c. Bootstrapped mode

```


--- AC Analysis ---
frequency:      1000      Hz
V(n003):        mag:      0.1 phase:      0°      voltage
V(vi):          mag: 0.0010878 phase: 0.197659° voltage
V(n001):        mag: 0.0010878 phase: 0.10647° voltage
V(p001):        mag: 0.000412828 phase: 0.10647° voltage
V(vc):          mag:      0 phase:      0°      voltage
V(ve):          mag: 0.00143612 phase: 0.11993° voltage
V(vo):          mag: 0.00146338 phase: -10.9158° voltage
V(n002):        mag: 0.00143612 phase: 0.121356° voltage
Ic(Q1):         mag: 1.70544e-005 phase: -179.838° device_current
Ib(Q1):         mag: 1.70544e-007 phase: -179.838° device_current
Ie(Q1):         mag: 1.7225e-005 phase: 0.161967° device_current
I(C2):          mag: 7.41101e-009 phase: 0.167846° device_current
I(Cc):          mag: 1.76006e-005 phase: 0.16109° device_current
I(C):           mag: 1.0878e-007 phase: 0.197659° device_current
I(R4):          mag: 7.41101e-009 phase: 0.167846° device_current
I(Re):          mag: 3.68236e-007 phase: 0.11993° device_current
I(R3):          mag: 4.12828e-008 phase: -179.894° device_current
I(R1):          mag: 1.76006e-005 phase: -179.839° device_current
I(R1):          mag: 4.12828e-008 phase: -179.894° device_current
I(R2):          mag: 2.78924e-008 phase: 0.10647° device_current
I(Rs):          mag: 1.0878e-007 phase: 0.197659° device_current
I(Vcc):         mag: 1.70957e-005 phase: 0.161833° device_current
I(Vs):          mag: 1.76006e-005 phase: -179.839° device_current

```


Rout = V(vout)/I(Vs) = 83.143 Ω

6. Input and Output Waveforms


a. For Common Collector Configuration

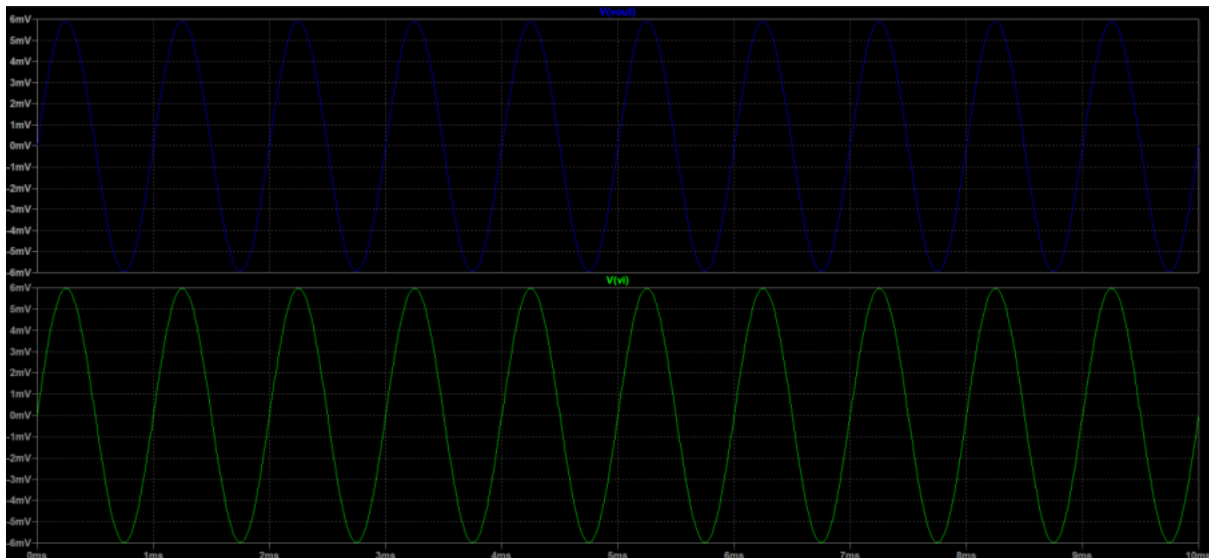

b. Darlington Pair

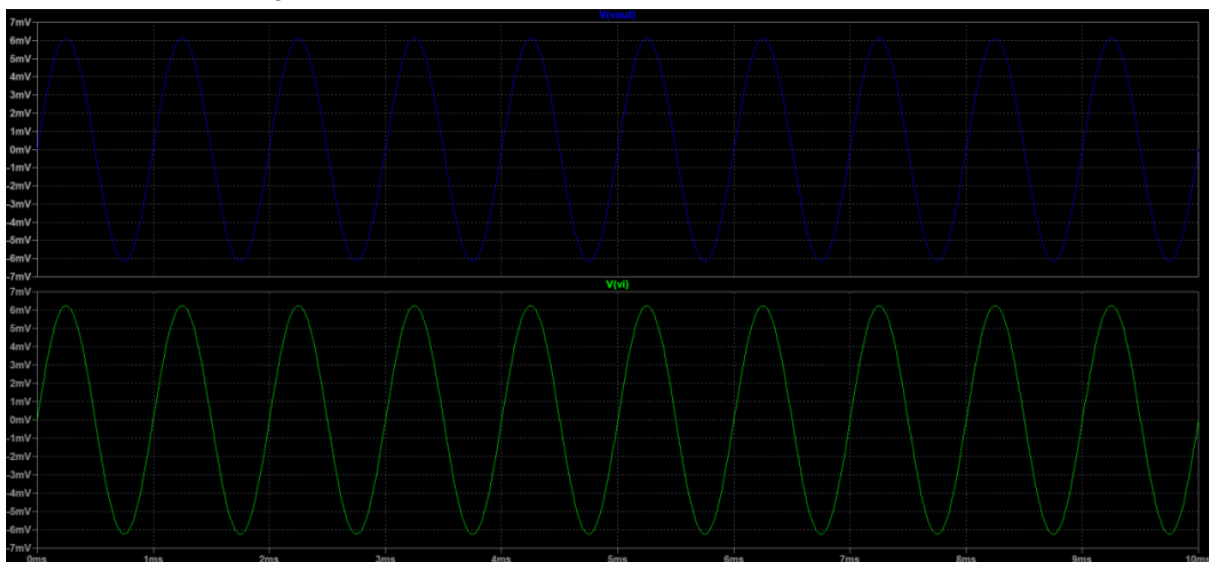

c. Bootstrapped mode

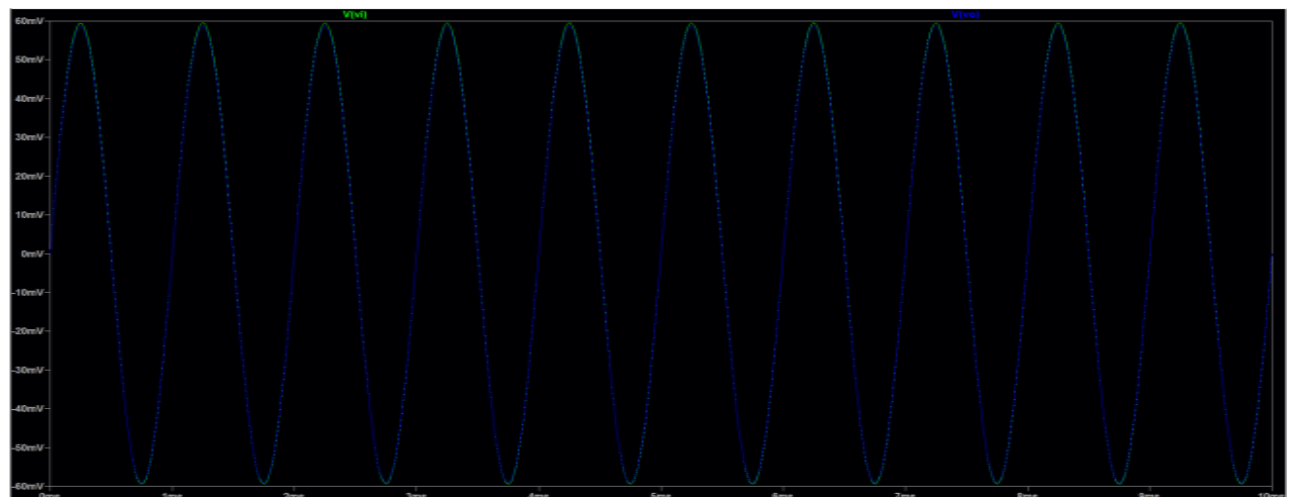

7. LTSpice Net lists

A. common collector configuration

```
* E:\BITS Pilani\3-2\AnE\Labs\Lab2.asc

V1 P001 0 SINE(0 10m 1k) AC 10m 0

V2 Vc 0 10

R1 N003 P001 10k

R2 Vc N002 10k

R3 N002 N004 {R}

R4 N004 0 39k

R5 Ve 0 3.9k

R6 N001 0 5.6k

C1 N003 N004 10μ

C2 N001 Ve 10μ

Q1 Vc N004 Ve 0 NPN

.model NPN NPN

.model PNP PNP

.lib C:\Users\Jash Shah\Documents\LTspiceXVII\lib\cmp\standard.bjt

.step param R 1k 50k 1k

.op

* Common Collector amplifier Schematic

.backanno

.end
```

B. Darlington Pair

```
* E:\BITS Pilani\3-2\AnE\Labs\Lab2.asc

V1 P001 0 SINE(0 10m 1k) AC 10m 0

V2 Vc 0 10

R1 N003 P001 10k

R2 Vc N002 10k

R3 N002 N004 {R}

R4 N004 0 39k

R5 Ve 0 3.9k

R6 N001 0 5.6k

C1 N003 N004 10μ

C2 N001 Ve 10μ

Q1 Vc N005 Ve 0 NPN

Q2 Vc N004 N005 0 NPN

.model NPN NPN

.model PNP PNP

.lib C:\Users\Jash Shah\Documents\LTspiceXVII\lib\cmp\standard.bjt

.step param R 1k 50k 1k

.op

* Darlington mode

.backanno

.end
```

C. Bootstrapped emitter follower

```
* E:\BITS Pilani\3-2\AnE\Labs\Lab2.asc

V1 P001 0 SINE(0 10m 1k) AC 10m 0

V2 Vc 0 10

R1 N003 P001 10k
```

```
R2 Vc N002 10k

R3 N002 N004 {R}

R4 N004 0 39k

R5 Ve 0 3.9k

R6 N001 0 5.6k

C1 N003 N004 10μ

C2 N001 Ve 10μ

Q1 Vc N004 Ve 0 NPN

R7 N005 N004 47K

C3 Ve N005 33μ

.model NPN NPN

.model PNP PNP

.lib C:\Users\Jash Shah\Documents\LTspiceXVII\lib\cmp\standard.bjt

.step param R 1k 50k 1k

.op

* Bootstrapped configuration

.backanno

.end
```