

To Study active filters characteristics using OPAMP (IC-741)

Analog Electronics Lab Experiment -6

Submitted by : Jash Shah

BITS Id : 2018A8PS0507P

Lab Section: P5

Submitted to : Sambhavi Shukla, Teena Gakhar

Date : 27/2/21

1. Objective

To study the Active Filters using OP AMP (IC-741)

- 1) Low Pass Filter
- 2) High Pass Filter
- 3) Band Pass Filter

Report the following:


- 1) Circuit diagrams for all three configurations.
- 2) Plot the Voltage Gain versus Frequency for all the three types of active Filters .
- 3) Calculate the 3-dB cut-off frequency and compare your simulated values with the theoretical ones in tabular form.

Assumptions:


- 1) Ideal behaviour of the OPAMP.
- 2) All the calculations to be done at 1kHz frequency.

2. Low Pass Filter

1. Circuit Diagram:

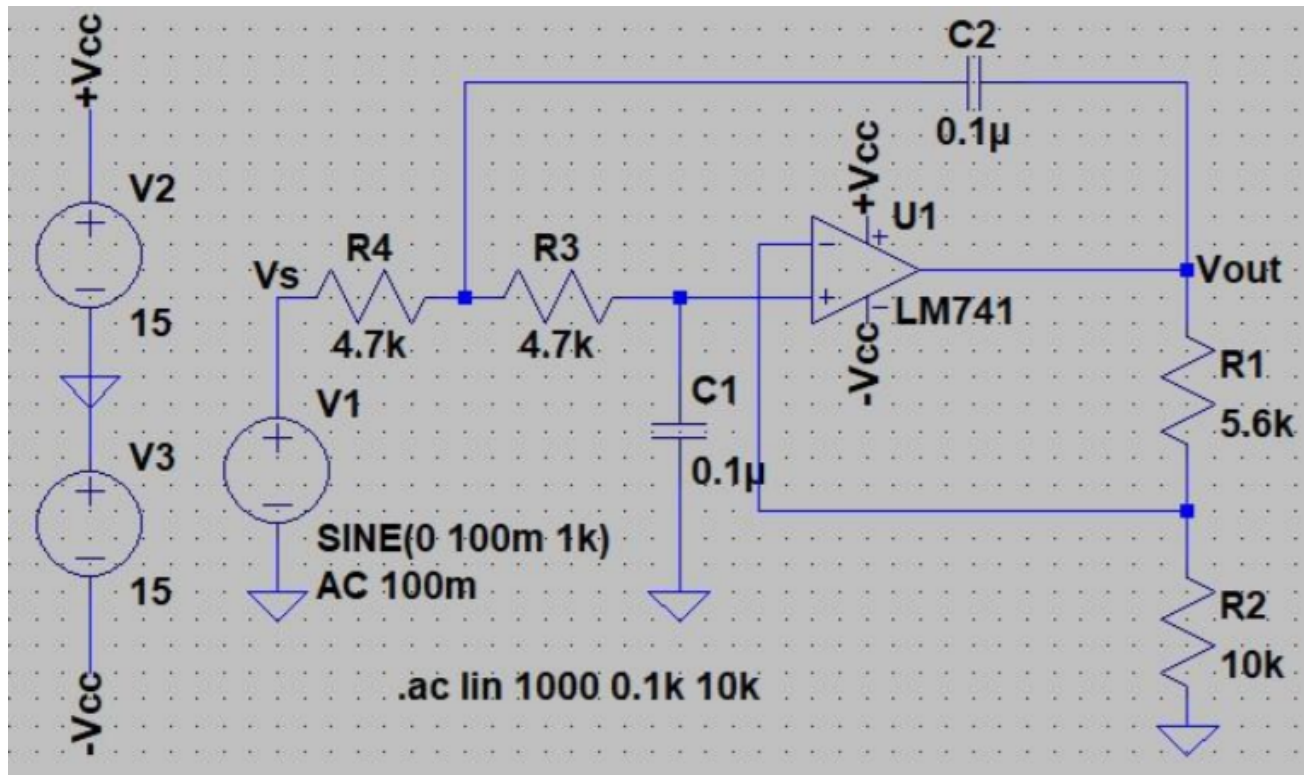

2. Resultant Curve and simulation result

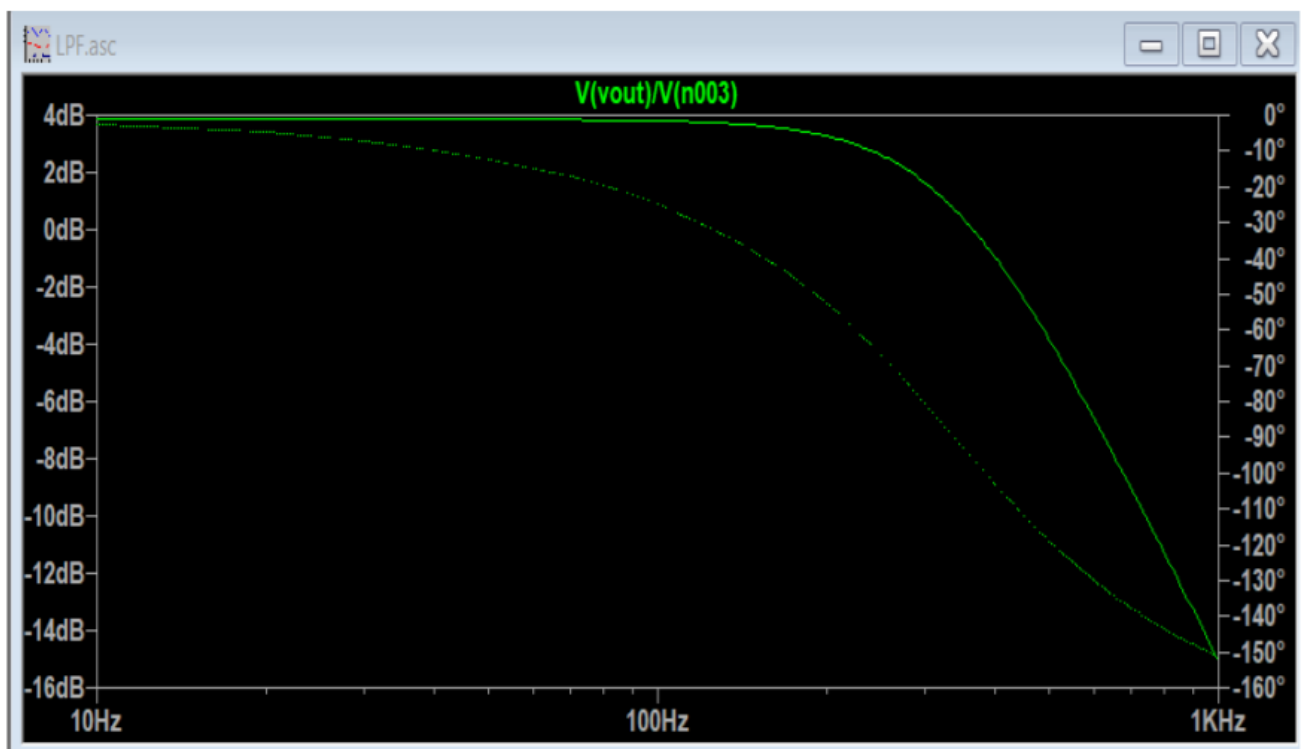

Simulated Value of $f_{3dB} = 331.13 \text{ Hz}$

Simulated value of $A_v = 3.863$ dB

3. Hand Calculations


Theoretically, the cutoff frequency is given as: $f_{o,th} = 1/(2 \cdot \pi \cdot (R_3 \cdot R_4 \cdot C_1 \cdot C_2)^{1/2})$; where R_3, R_4, C_1, C_2 are as per shown in the schematic.

So, $f_{o,th} = 338.6$ Hz.


And for A_v it is $20 \log((R_2 + R_1)/R_2) = 3.862$ dB

3. High Pass Filter

1. Circuit Diagram:

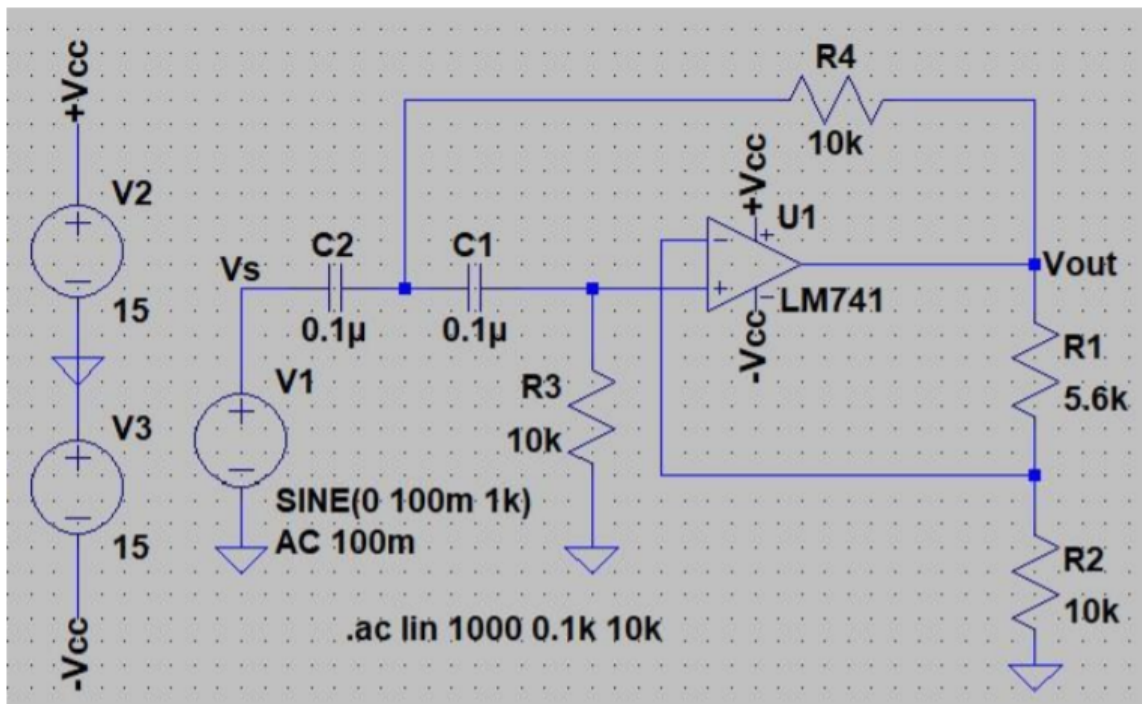

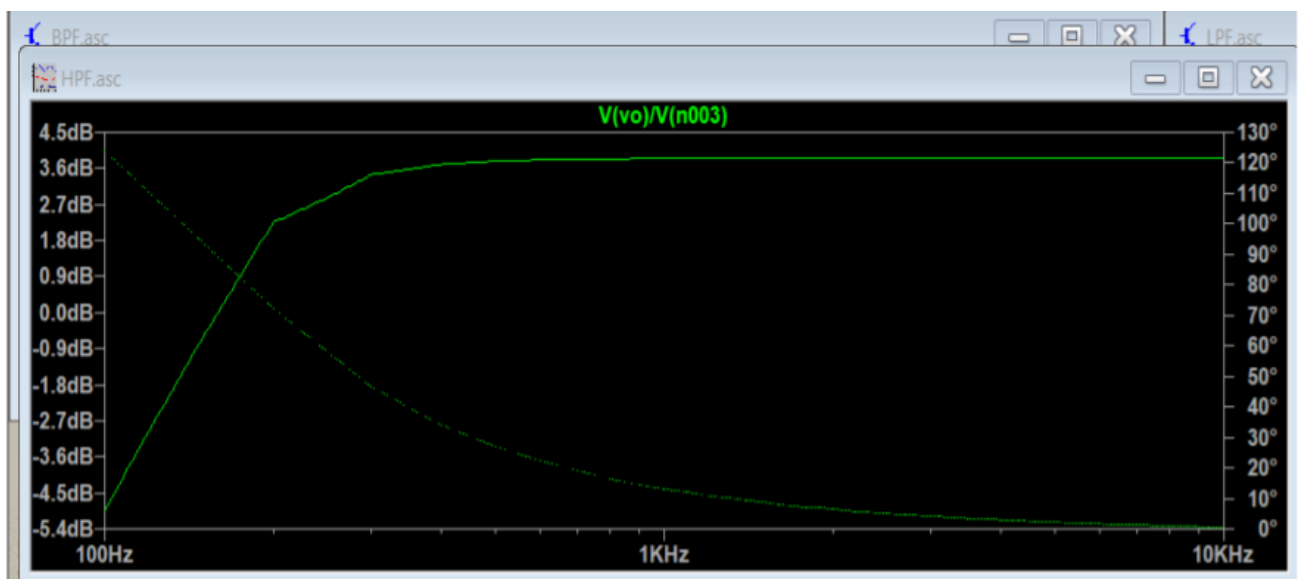2. Resultant analysis and simulated result



(Simulated) $f_{-3dB} = 162.28623$ Hz


(Theoretical) $f_{-3dB} = 159.15$ Hz

Formula for $F_{-3dB} = 1/\sqrt{R_1 R_2 C_1 C_2}$


A_v , high frequency = $20\log(R_2 + R_1/R_2) = 3.862 \text{ dB}$
 A_v simulated = 3.858 dB

4. Band Pass Filter

1. Circuit Diagram:

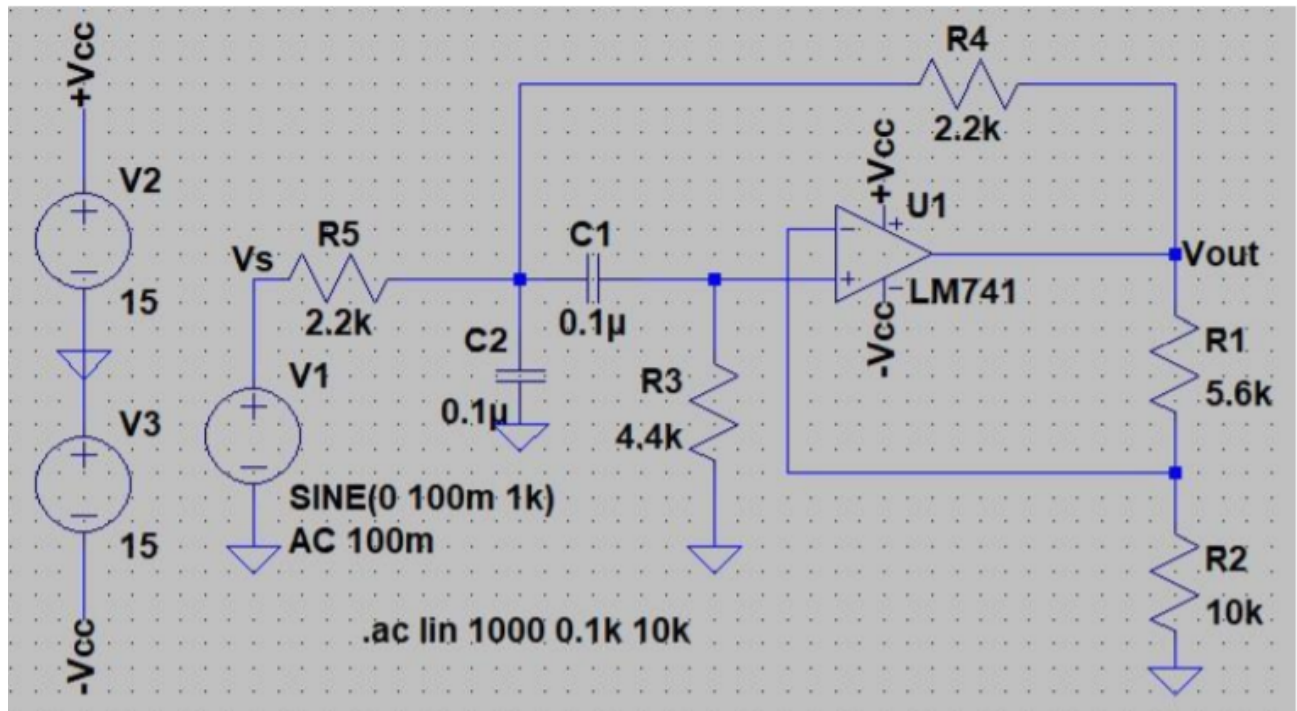

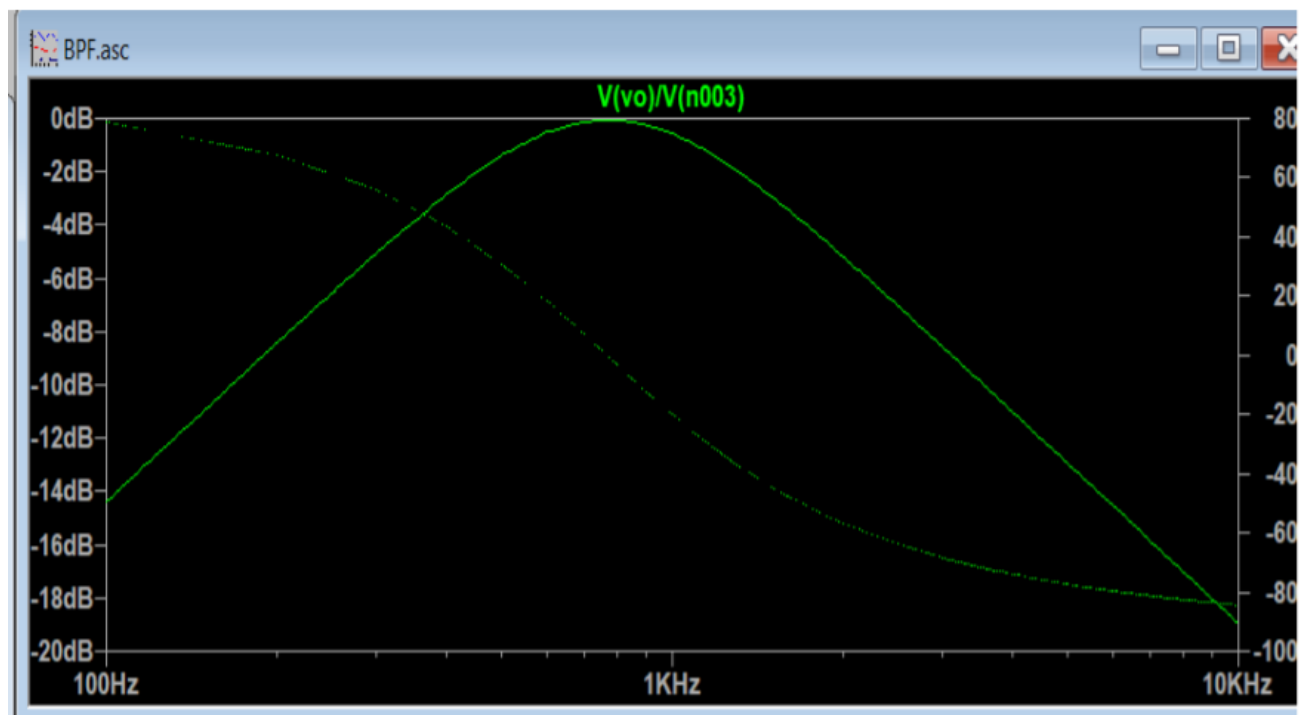2. Resultant analysis and simulation results



Maximum Amplitude of 696.1031 mdB at a frequency of 722.77228 Hz

Theoretically, the cutoff frequency is given as: $f_{o,th} = 1/(2 \cdot \pi \cdot R_4 \cdot C_1)$; where R_4, C_1 are as per shown in the schematic. Theoretical value at max $f = 723.43 \text{ Hz}$

$f_{-3\text{dB (lower)}} = 352.52588 \text{ Hz}$

f-3dB (higher) = 1.4831683KHz

For Av, the simulated value was to be 0.696 dB

And, in theory, $20\text{Log}((R2 + R1)/(2R2 - R1)) = 0.695 \text{ dB}$

5. Results

1. For 3-dB frequencies

Filter Type	Simulated fo (Hz)	Theoretical fo (Hz)
Low Pass	331.13	338.6
High Pass	162.28	159.15
Band Pass	722.77228 (Higher)	723.43 (Higher)

2. For Voltage gains

Filter Type	Simulated fo (dB)	Theoretical fo (dB)
Low Pass	3.863	3.862
High Pass	3.858	3.862
Band Pass	0.696	0.695