

# Study the basic configuration of OPAMP (IC-741)

## Analog Electronics Lab Experiment -3

**Submitted by :** Jash Shah

**BITS Id :** 2018A8PS0507P

**Lab Section:** P5

**Submitted to :** Sambhavi Shukla, Teena Gakhar

**Date :** 6/2/21

---

### **1. Objective**

To study the following basic configuration of an Operational Amplifier and verify the same using LTSpice simulation of IC 741:

- 1) Inverting Mode
- 2) Non-inverting mode
- 3) Adder
- 4) Subtractor


**Report the following:**

- 1) Circuit diagrams for all four configurations.
- 2) Simulated and theoretical values of voltage gain ( $A_v$ ) and input-output voltage waveforms with magnitude for inverting and non-inverting mode.
- 3) Simulated and theoretical values of output voltage ( $V_o$ ) for adder
- 4) Simulated and theoretical values of output voltage ( $V_o$ ) for subtractor


**Assumptions:** Ideal behaviour of the OPAMP.

## 2. Schematic


### A. Inverting Amplifier :

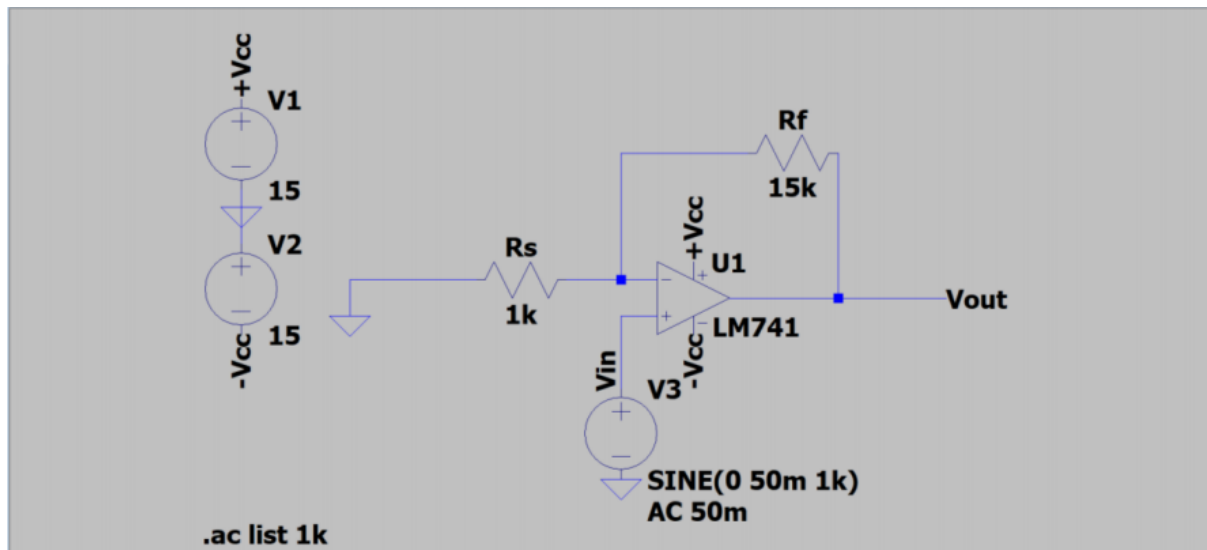


### B. Non-inverting Amplifier :

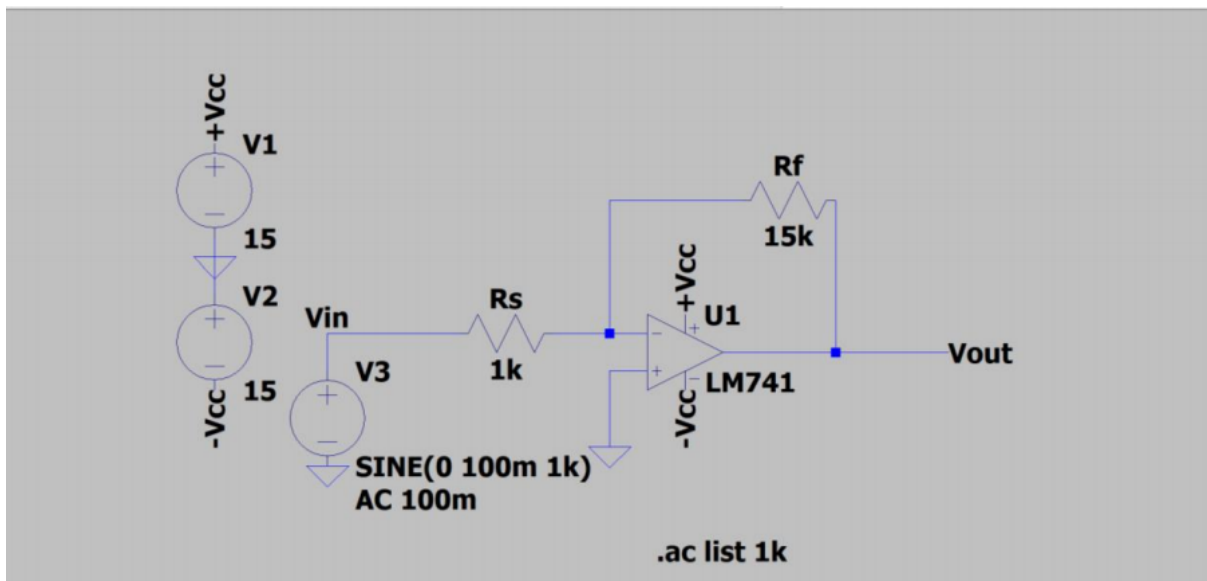

C. Adder circuit :

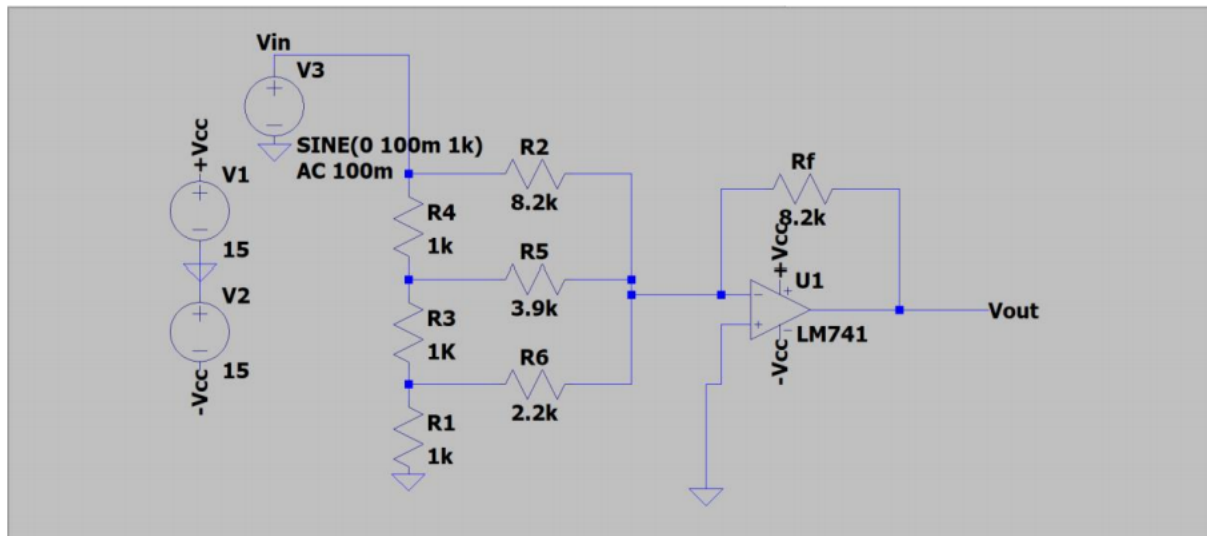

D. Subtractor circuit :

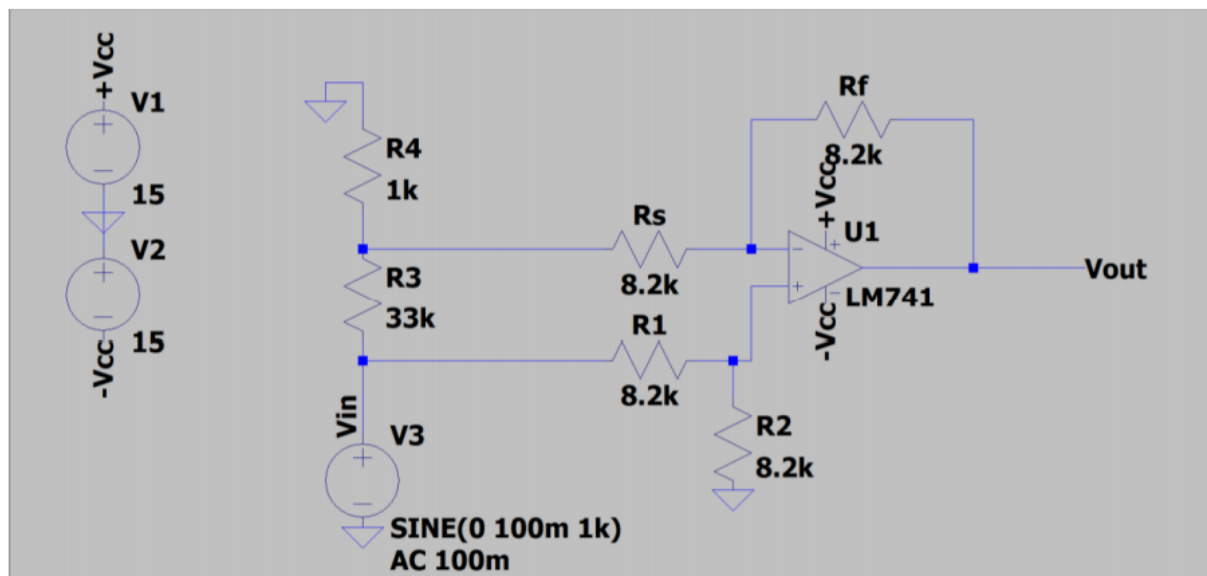

### 3. Volage Gain

#### A. Inverting Amplifier :

---

--- AC Analysis ---					
frequency:	1000	Hz			
V(n001):	mag: 0.000758591	phase: 88.8112°		voltage	
V(vs):	mag: 0.05	phase: 0°		voltage	
V(vout):	mag: 0.749846	phase: 179.07°		voltage	
V(-vcc):	mag: 0	phase: 0°		voltage	
V(+vcc):	mag: 0	phase: 0°		voltage	
I(Rf):	mag: 4.999e-005	phase: 179.128°		device_current	
I(Rs):	mag: 4.999e-005	phase: 179.131°		device_current	
I(V2):	mag: 2.48267e-005	phase: 179.128°		device_current	
I(V1):	mag: 2.51633e-005	phase: -0.872383°		device_current	
I(Vs):	mag: 4.999e-005	phase: 179.131°		device_current	
Ix(u1:1):	mag: 2.68845e-009	phase: -91.1901°		subckt_current	
Ix(u1:2):	mag: 2.68845e-009	phase: 88.8099°		subckt_current	
Ix(u1:99):	mag: 2.51633e-005	phase: 179.128°		subckt_current	
Ix(u1:50):	mag: 2.48267e-005	phase: 179.128°		subckt_current	
Ix(u1:28):	mag: 4.999e-005	phase: -0.872383°		subckt_current	

$$\text{Practical Gain} = V(\text{vout})/V(\text{vs}) = 0.749846/0.05 = -14.98692$$

$$\text{Theoretical Gain} = R_f/R_s = 15k/1k = -15$$

#### B. Non-Inverting Amplifier :

AC analysis at 1kHz (to calculate gain  $A_v$ ):

---


--- AC Analysis ---					
frequency:	1000	Hz			
V(n001):	mag: 0.0499913	phase: -0.920529°		voltage	
V(vout):	mag: 0.799861	phase: -0.923597°		voltage	
V(vs):	mag: 0.05	phase: 0°		voltage	
V(-vcc):	mag: 0	phase: 0°		voltage	
V(+vcc):	mag: 0	phase: 0°		voltage	
I(Rf):	mag: 4.99913e-005	phase: -0.923802°		device_current	
I(Rs):	mag: 4.99913e-005	phase: -0.920529°		device_current	
I(Vs):	mag: 2.85502e-009	phase: -91.126°		device_current	
I(V2):	mag: 2.48274e-005	phase: -0.923802°		device_current	
I(V1):	mag: 2.51639e-005	phase: 179.076°		device_current	
Ix(u1:1):	mag: 2.85502e-009	phase: 88.874°		subckt_current	
Ix(u1:2):	mag: 2.85501e-009	phase: -91.124°		subckt_current	
Ix(u1:99):	mag: 2.51639e-005	phase: -0.923802°		subckt_current	
Ix(u1:50):	mag: 2.48274e-005	phase: -0.923802°		subckt_current	
Ix(u1:28):	mag: 4.99913e-005	phase: 179.076°		subckt_current	

$$\text{Practical Gain} = V(\text{vout})/V(\text{vs}) = 0.79986/0.05 = 15.9892$$


$$\text{Theoretical Gain} = 1+(R_f/R_s) = 1+15k/1k = 1+15 = 16$$

## 4. Input and Output Waveforms

### A. Inverting Amplifier :

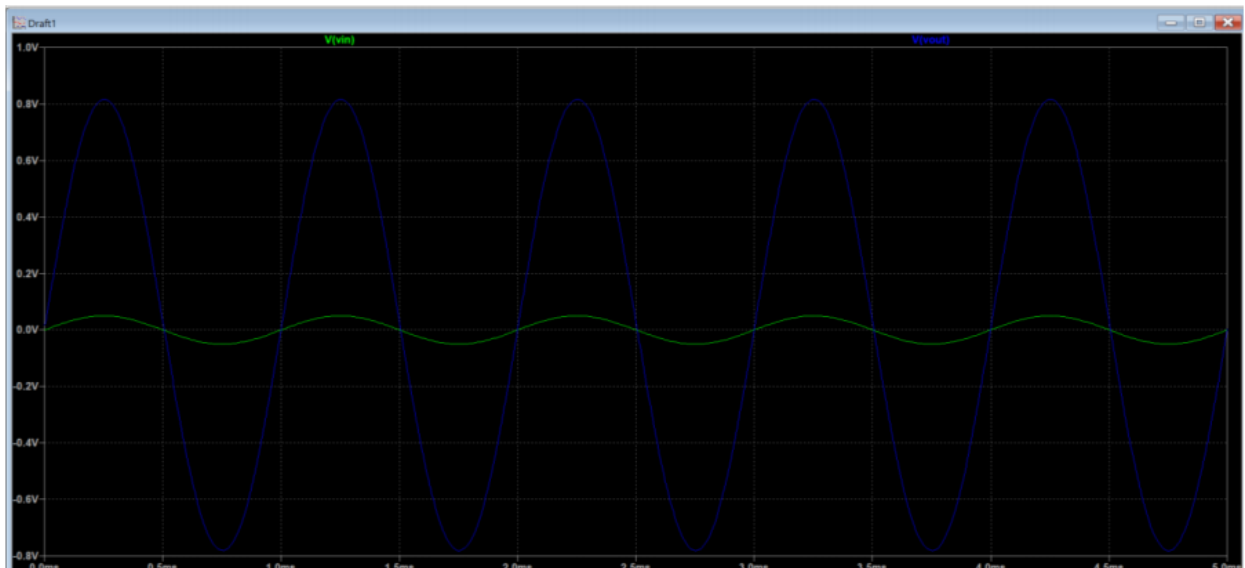

### B. Non-Inverting Amplifier :

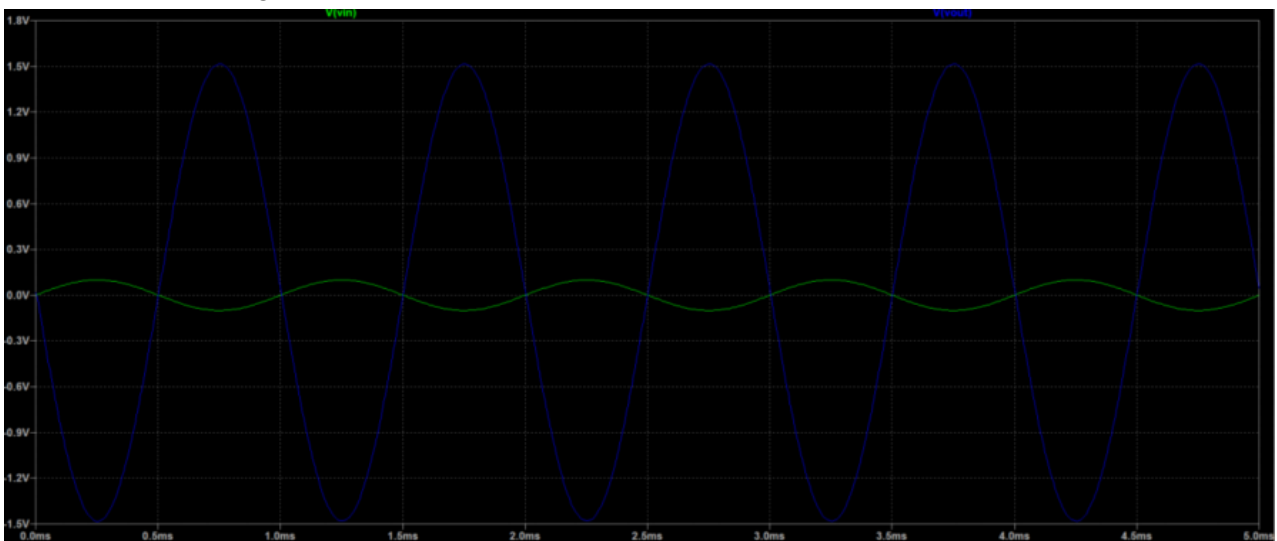

## 5. Output Voltages

### A. Adder Circuit :

--- AC Analysis ---				
frequency:	1000	Hz		
V(n001):	mag: 0.000302253	phase: 89.3731°	voltage	
V(-vcc):	mag: 0	phase: 0°	voltage	
V(+vcc):	mag: 0	phase: 0°	voltage	
V(vout):	mag: 0.295825	phase: 179.631°	voltage	
V(v1):	mag: 0.1	phase: 0°	voltage	
V(v2):	mag: 0.054084	phase: 0.076469°	voltage	
V(v3):	mag: 0.022035	phase: 0.222°	voltage	
I(R6):	mag: 2.2035e-005	phase: 0.222°	device_current	
I(R5):	mag: 3.20492e-005	phase: -0.0235887°	device_current	
I(R4):	mag: 4.59161e-005	phase: -0.090072°	device_current	
I(R3):	mag: 1.00148e-005	phase: 179.436°	device_current	
I(R2):	mag: 1.3867e-005	phase: 179.756°	device_current	
I(R1):	mag: 1.21948e-005	phase: 179.827°	device_current	
I(Rf):	mag: 3.60764e-005	phase: 179.69°	device_current	
I(Vs):	mag: 5.81108e-005	phase: 179.892°	device_current	
I(V2):	mag: 1.79561e-005	phase: 179.69°	device_current	
I(V1):	mag: 1.81203e-005	phase: -0.310472°	device_current	
Ix(u1:1):	mag: 1.07119e-009	phase: -90.6282°	subckt_current	
Ix(u1:2):	mag: 1.07119e-009	phase: 89.3718°	subckt_current	
Ix(u1:99):	mag: 1.81203e-005	phase: 179.69°	subckt_current	
Ix(u1:50):	mag: 1.79561e-005	phase: 179.69°	subckt_current	
Ix(u1:28):	mag: 3.60764e-005	phase: -0.310472°	subckt_current	

Practical Vout(V(vout)) = 0.295825V

Theoretical Vout =  $\{(Rf/R1)*V1 + (Rf/R2)*V2 + (Rf/R3)*V3\} = \{1*0.1 + 2.102*0.054 + 3.72*0.02\} = 0.295584V$

### B. Subtractor circuit :

--- AC Analysis ---				
frequency:	1000	Hz		
V(n001):	mag: 0.0500011	phase: -0.101991°	voltage	
V(n002):	mag: 0.05	phase: -0.00149847°	voltage	
V(-vcc):	mag: 0	phase: 0°	voltage	
V(+vcc):	mag: 0	phase: 0°	voltage	
V(vout):	mag: 0.0920803	phase: -0.106532°	voltage	
V(v2):	mag: 0.00792186	phase: -0.0681324°	voltage	
V(v1):	mag: 0.1	phase: 0°	voltage	
I(R6):	mag: 7.92186e-006	phase: 179.932°	device_current	
I(R5):	mag: 2.79025e-006	phase: -179.994°	device_current	
I(R4):	mag: 6.09756e-006	phase: -0.00149847°	device_current	
I(R3):	mag: 6.09756e-006	phase: -179.999°	device_current	
I(R2):	mag: 5.13161e-006	phase: -0.108366°	device_current	
I(Rf):	mag: 5.13161e-006	phase: -0.111927°	device_current	
I(V2):	mag: 2.56291e-006	phase: -0.111927°	device_current	
I(V1):	mag: 2.56871e-006	phase: 179.888°	device_current	
I(Vs):	mag: 8.88781e-006	phase: -179.997°	device_current	
Ix(u1:1):	mag: 3.18942e-010	phase: 90.1799°	subckt_current	
Ix(u1:2):	mag: 3.18943e-010	phase: -89.8021°	subckt_current	
Ix(u1:99):	mag: 2.56871e-006	phase: -0.111927°	subckt_current	
Ix(u1:50):	mag: 2.56291e-006	phase: -0.111927°	subckt_current	
Ix(u1:28):	mag: 5.13161e-006	phase: 179.888°	subckt_current	

Practical Vout(V(vout)) = 0.0920803V

Theoretical Vout =  $(Rf/R1)*(V1-V2) = 1*(0.1-0.00792186) = 0.09207814$